
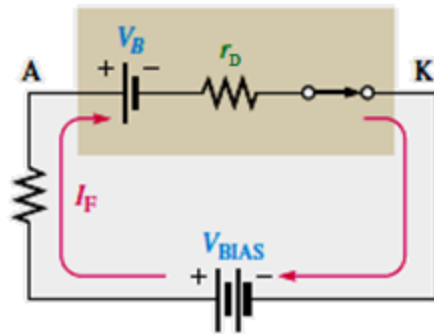


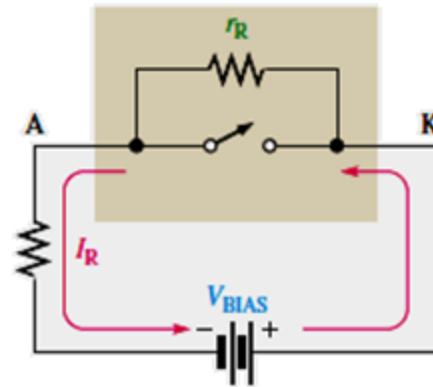


# The Complete diode model




(a) Forward bias



(b) Reverse bias

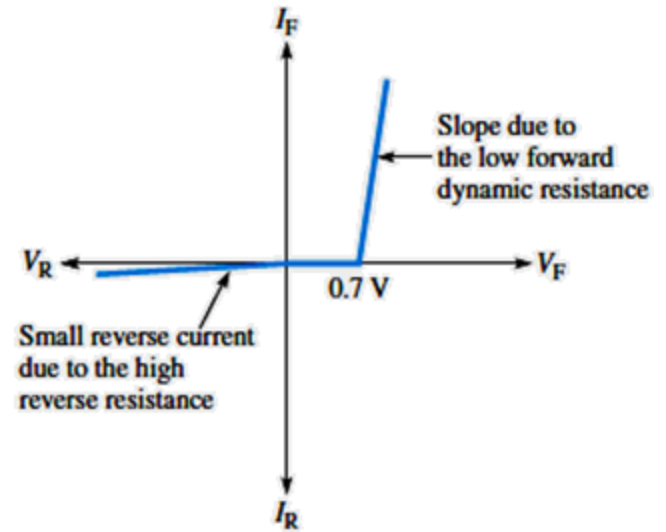


(c)  $V$ - $I$  characteristic curve

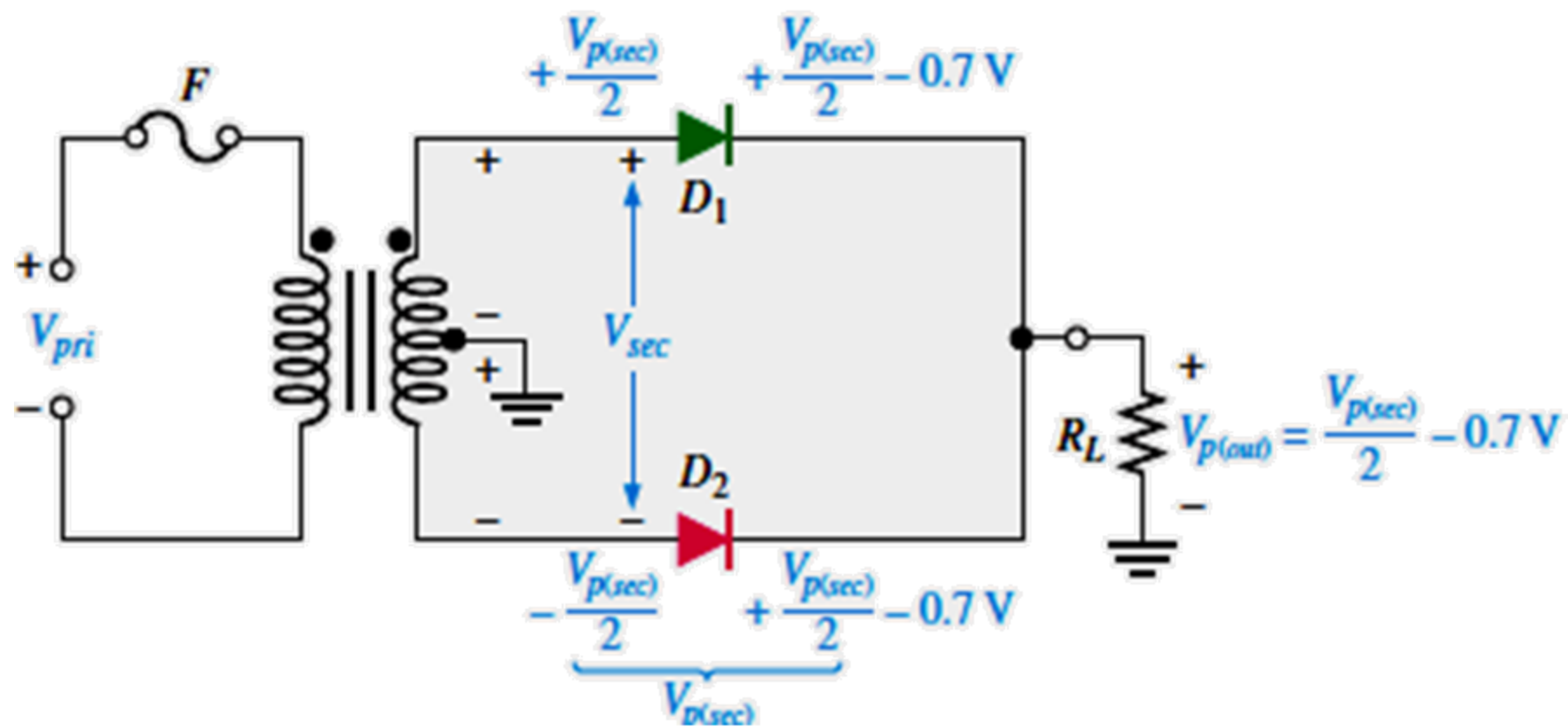

Transformer coupling provides two advantages.

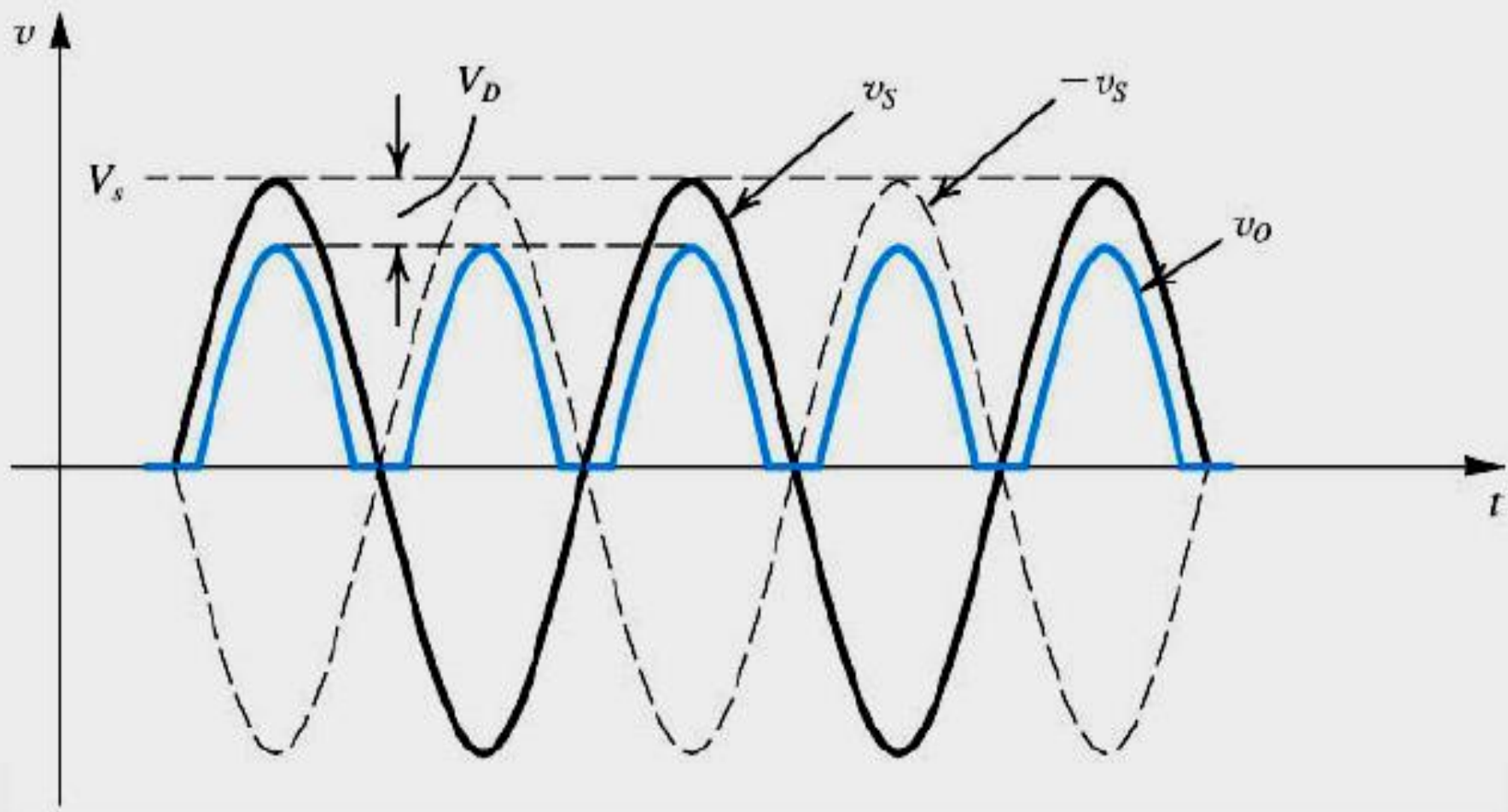- First, it allows the source voltage to be stepped down as needed.
- Second, the ac source is electrically isolated from the rectifier, thus preventing a shock hazard in the secondary circuit.



(c) input and output waveforms.


# Bridge rectifier

## Advantages :


- **No center tap is required** in the transformer secondary so in case of a bridge rectifier the transformer required is **simpler**. If stepping up or stepping down of voltage is not required, transformer can be eliminated even.
- For a given power output, **power transformer of smaller size can be used** in case of the bridge rectifier because current in both primary and secondary windings of the supply transformer flow for the entire ac cycle.
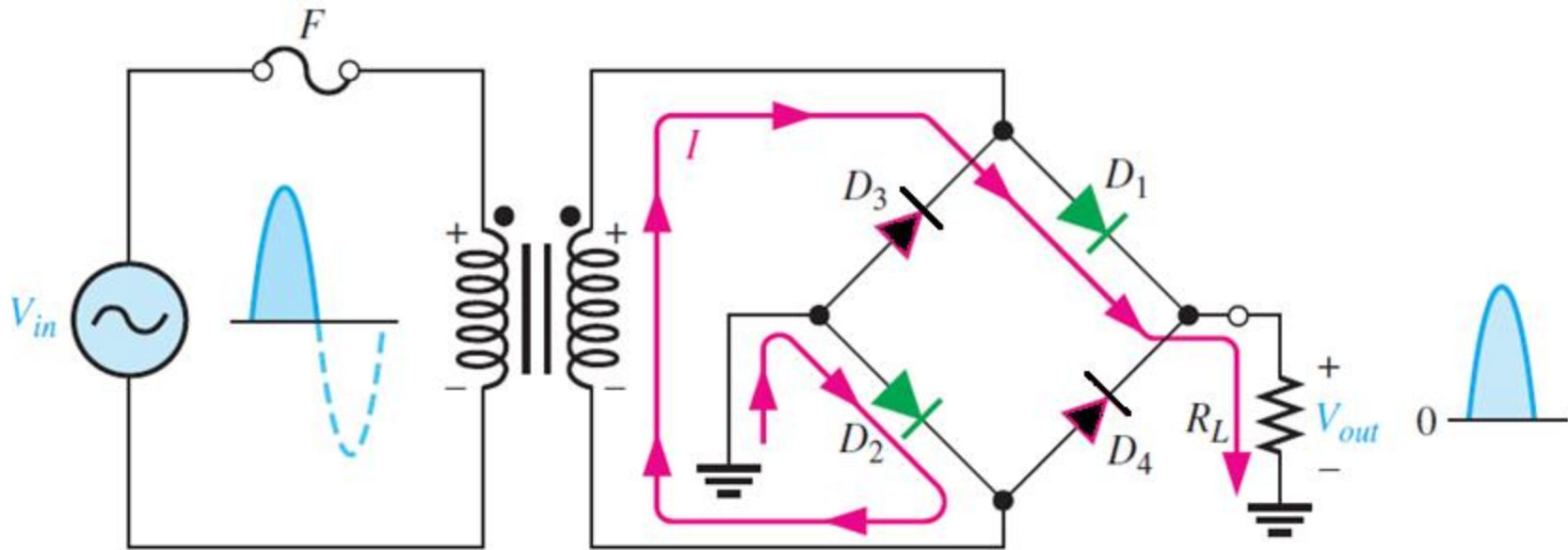
## Disadvantages:

- It requires **four diodes**.
- The use of two extra diodes cause an **additional voltage drop** thereby reducing the output voltage



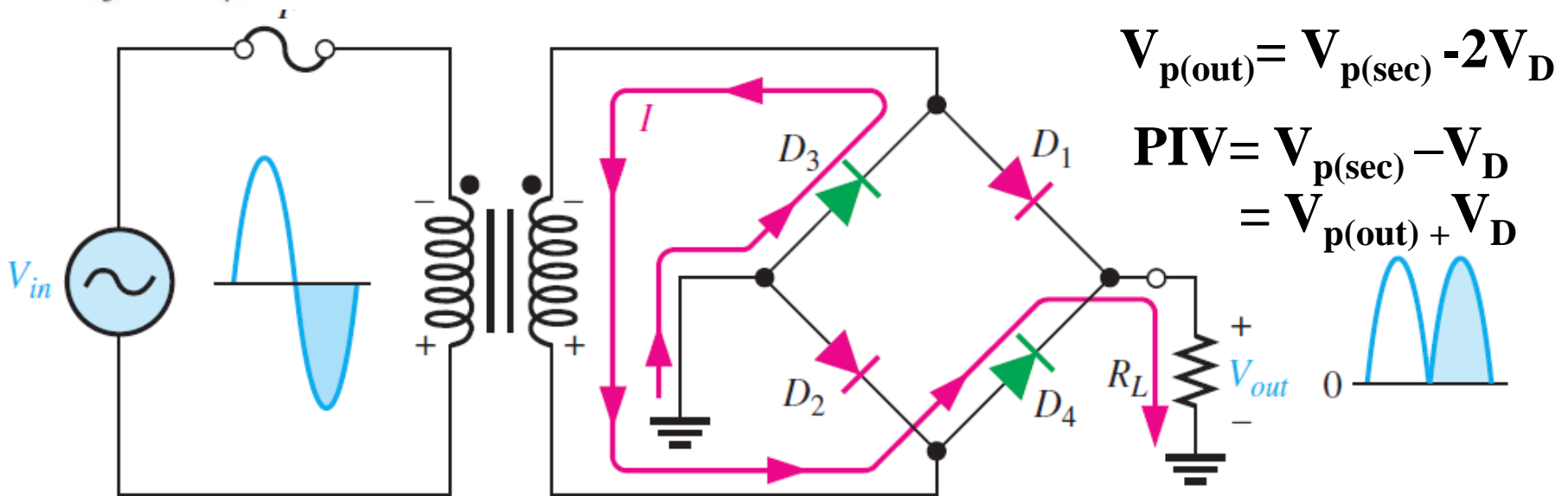(a) During the positive half-cycle of the input,  $D_1$  and  $D_2$  are forward-biased and conduct current.  $D_3$  and  $D_4$  are reverse-biased.



(b) During the negative half-cycle of the input,  $D_3$  and  $D_4$  are forward-biased and conduct current.  $D_1$  and  $D_2$  are reverse-biased.

We assume  $v_s = V_m \sin \alpha$  thus

$$\begin{aligned} V_{DC} &= 2 \times \left\{ \frac{1}{2\pi} \int_0^\pi v_s d\alpha \right\} \\ &= \frac{2 \times 1}{2\pi} \int_0^\pi V_m \sin \alpha d\alpha \\ &= \frac{V_m}{\pi} (-\cos \alpha \Big|_0^\pi) \\ &= \frac{2 \times V_m}{\pi} = 0.636 V_m \end{aligned}$$

$$\begin{aligned} V_{rms} &= \left[ \frac{2 \times 1}{2\pi} \int_0^\pi v_s^2 d\alpha \right]^{1/2} \\ V_{rms}^2 &= \frac{2 \times 1}{2\pi} \int_0^\pi V_m^2 \sin^2 \alpha d\alpha \\ &= \frac{2 \times V_m^2}{2\pi} \int_0^\pi \left( \frac{1}{2} - \frac{1}{2} \cos 2\alpha \right) d\alpha \\ &= \frac{V_m^2}{\pi} \left( \frac{1}{2} \alpha - \frac{1}{4} \sin 2\alpha \right) \Big|_0^\pi \\ &= \frac{V_m^2}{2} \Rightarrow V_{rms} = 0.707 V_m \end{aligned}$$

- Ripple factor is a measure of effectiveness of a rectifier circuit and defined as a ratio of rms value of ac component to the dc component (voltage or current) in the rectifier output.

