
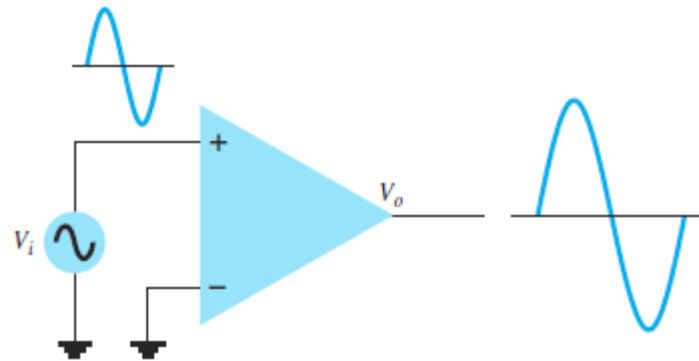



# Operational Amplifiers

## Op-Amp



CM


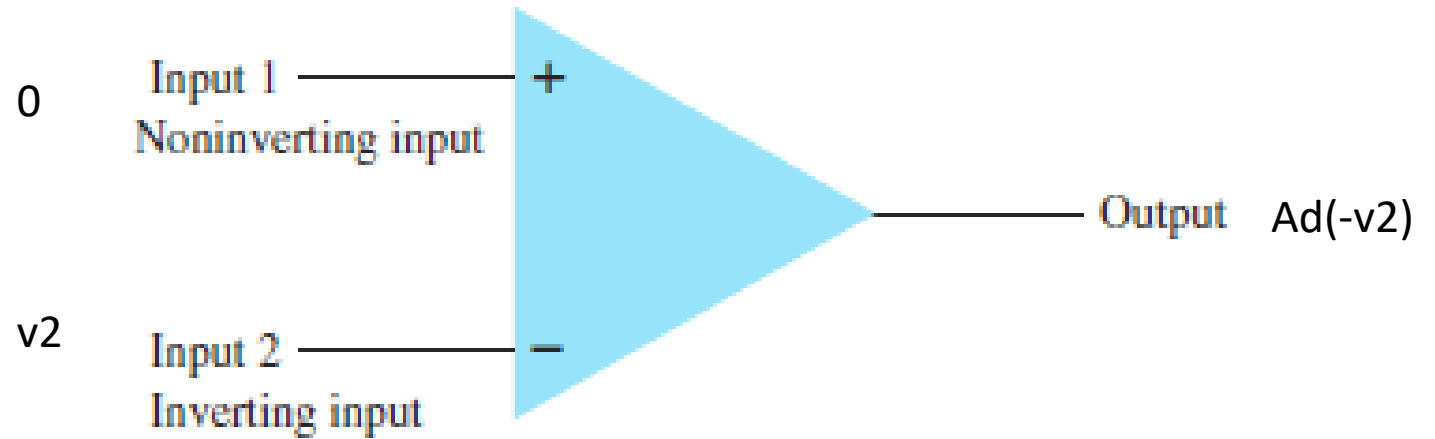


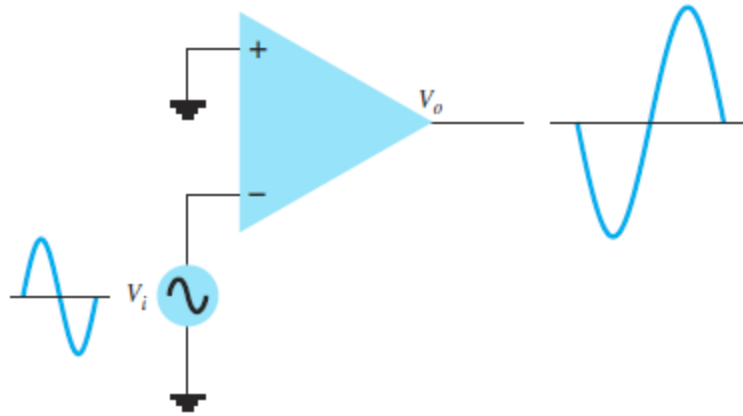$A_d=10^6$   
 $V_i=1V$   
 $V_{Omax}=\pm V_{CC}=\pm V_{sat}=15V$   
 $V_{mmax}=15\mu V$




*Double-ended (differential) operation*

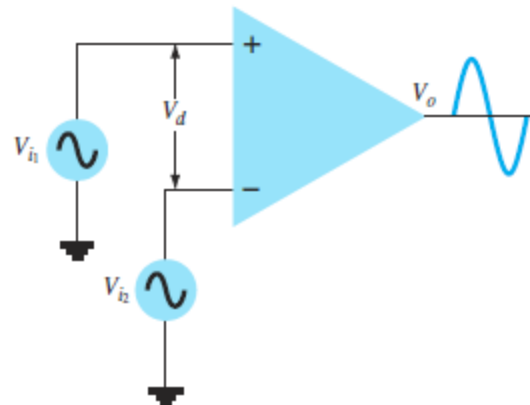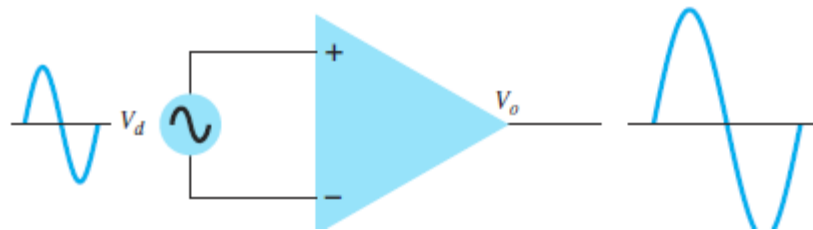


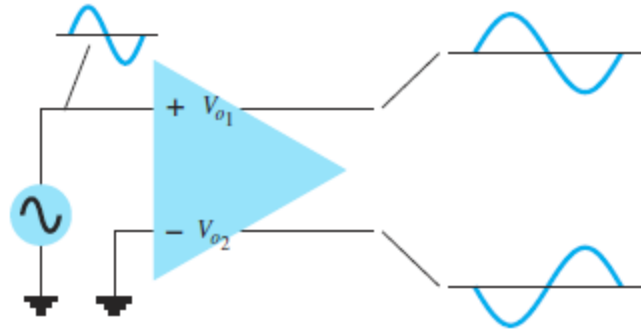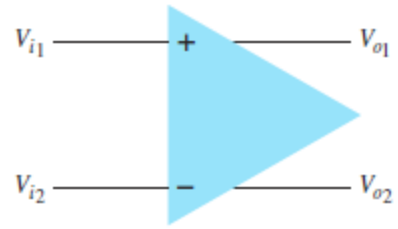


## Common-Mode Operation

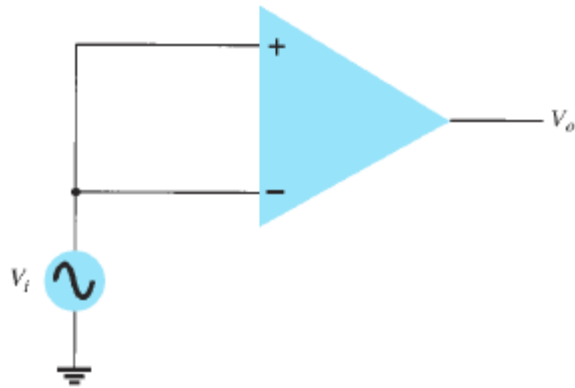

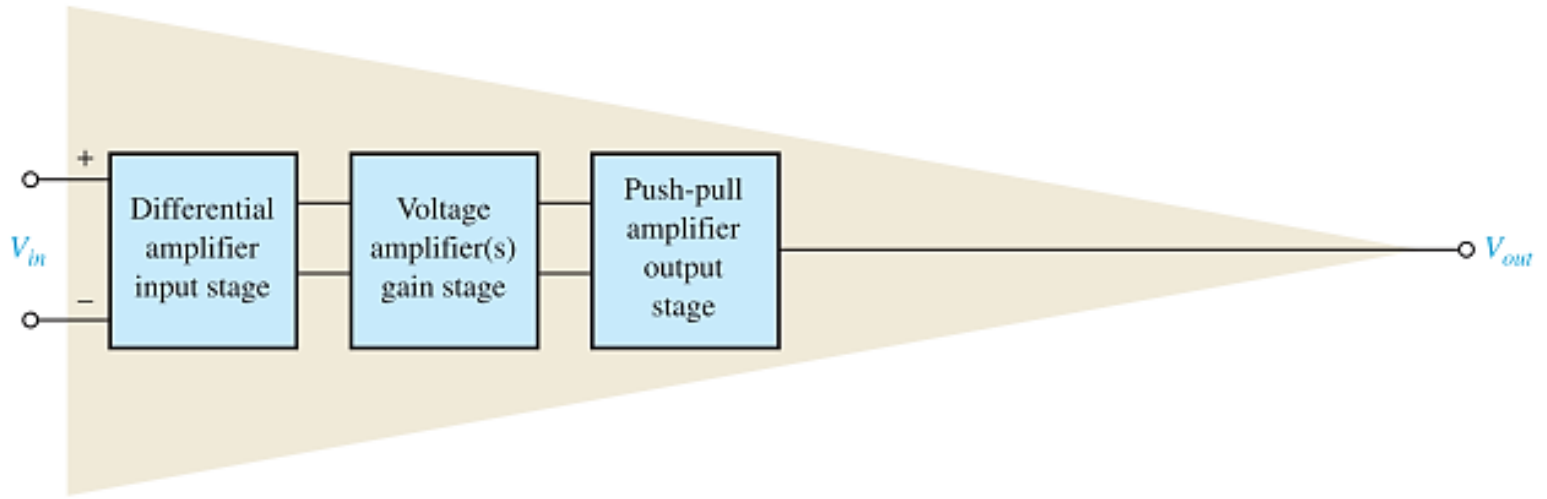
Common Mode Rejection Ratio (CMRR) =  $A_d/A_c = \infty$




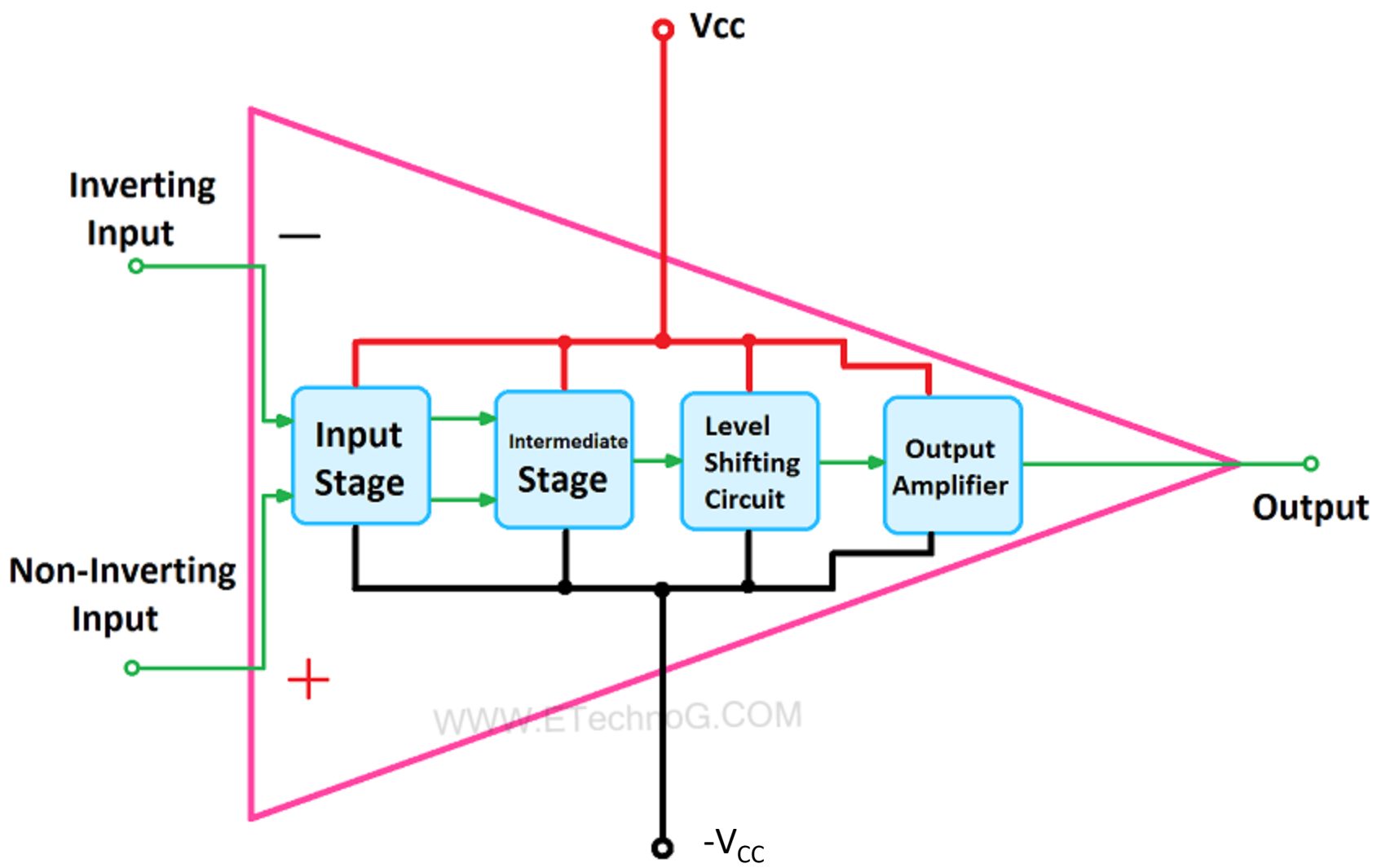

**Operational Amplifier or Op Amp Block Diagram**

# DIFFERENTIAL AMPLIFIER CIRCUIT

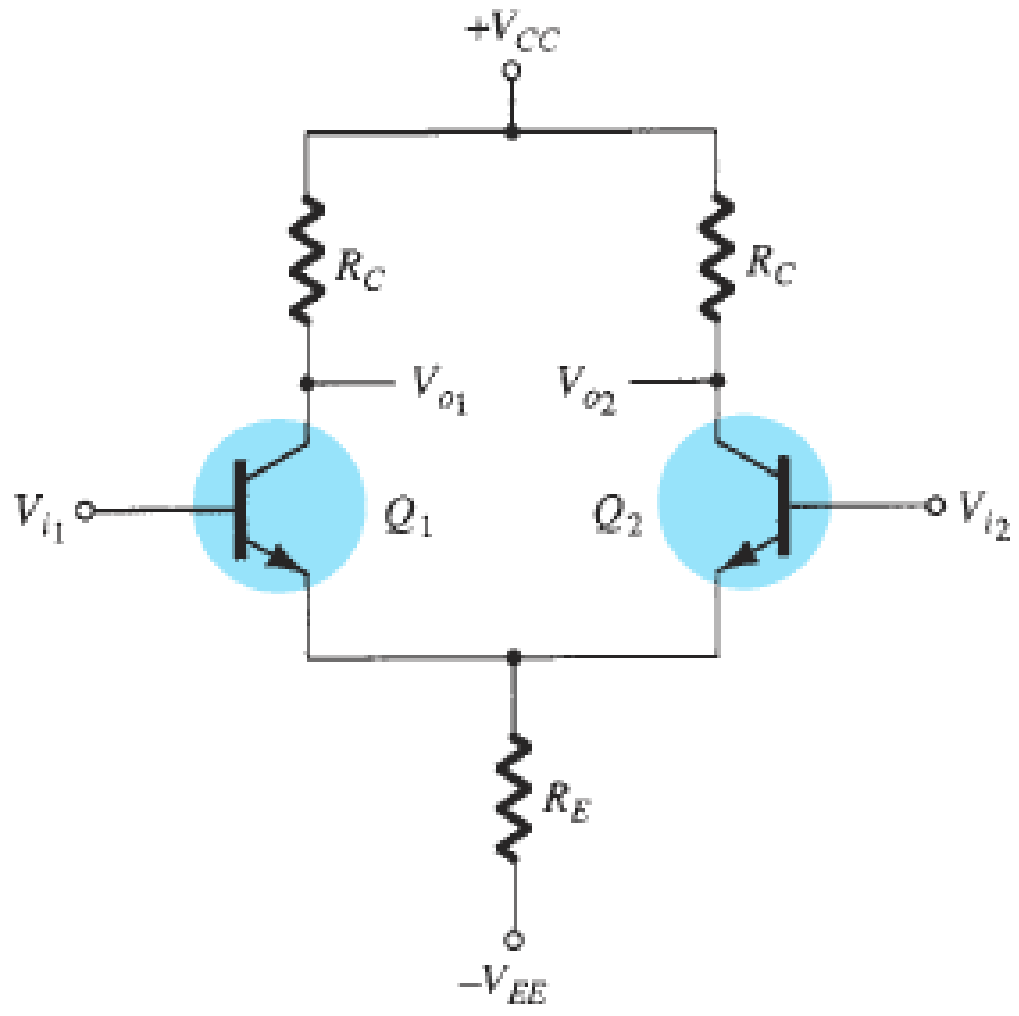


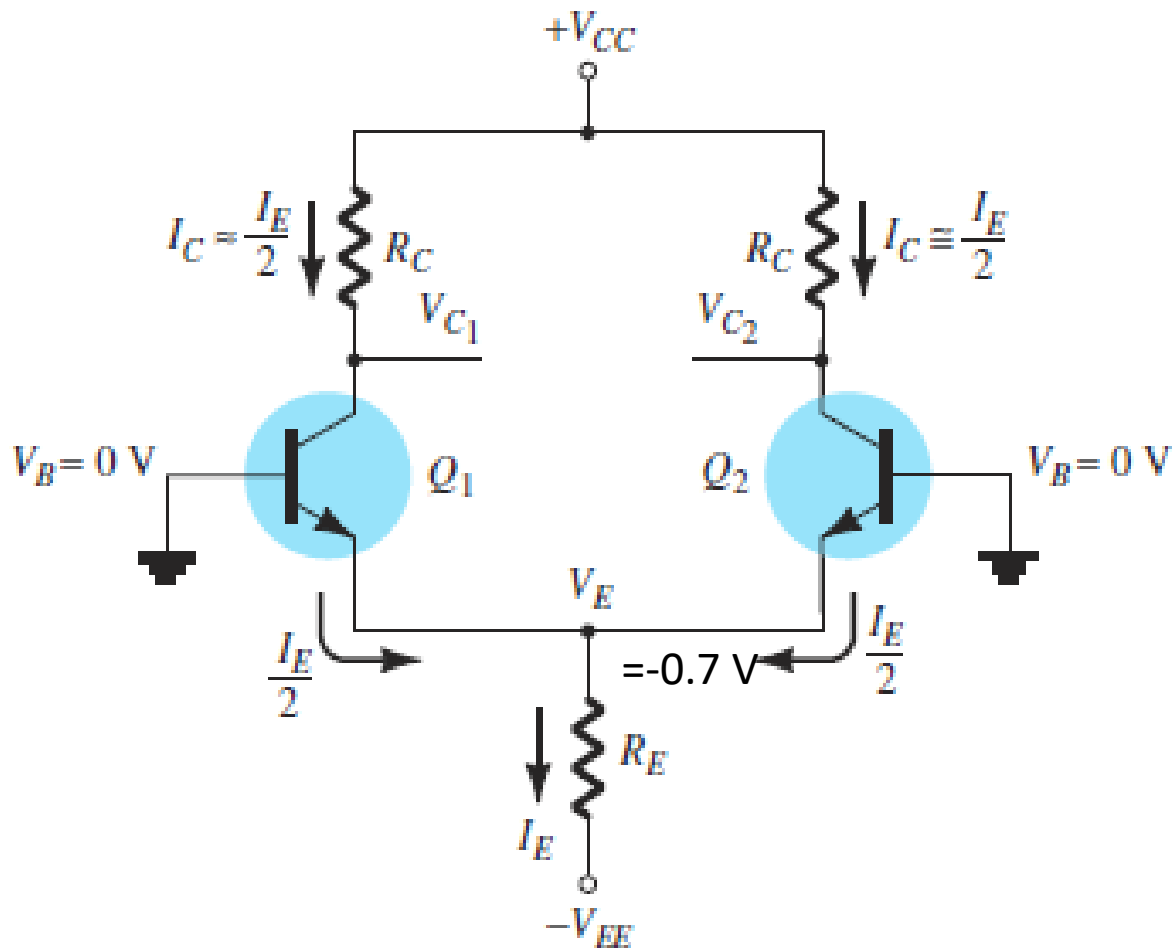

$$I_E = \frac{V_E - (-V_{EE})}{R_E} \approx \frac{V_{EE} - 0.7\text{ V}}{R_E}$$

$$V_{C_1} = V_{C_2} = V_{CC} - I_C R_C = V_{CC} - \frac{I_E}{2} R_C$$


( $V_{CC} - I_E/2 R_C$ ,  $I_E/2$ )

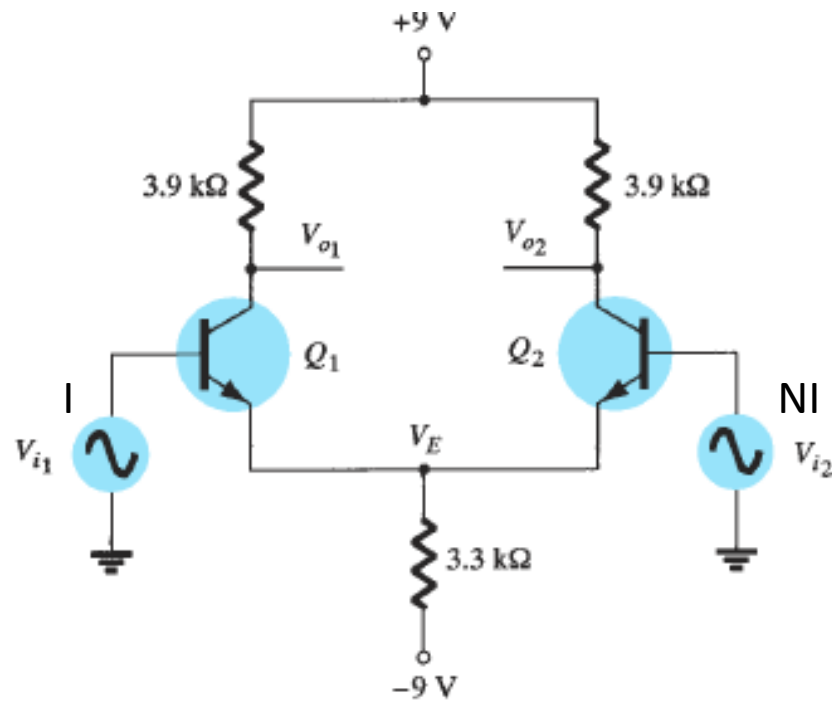


$$I_E = \frac{V_{EE} - 0.7 \text{ V}}{R_E} = \frac{9 \text{ V} - 0.7 \text{ V}}{3.3 \text{ k}\Omega} \approx 2.5 \text{ mA}$$

$$I_C = \frac{I_E}{2} = \frac{2.5 \text{ mA}}{2} = 1.25 \text{ mA}$$
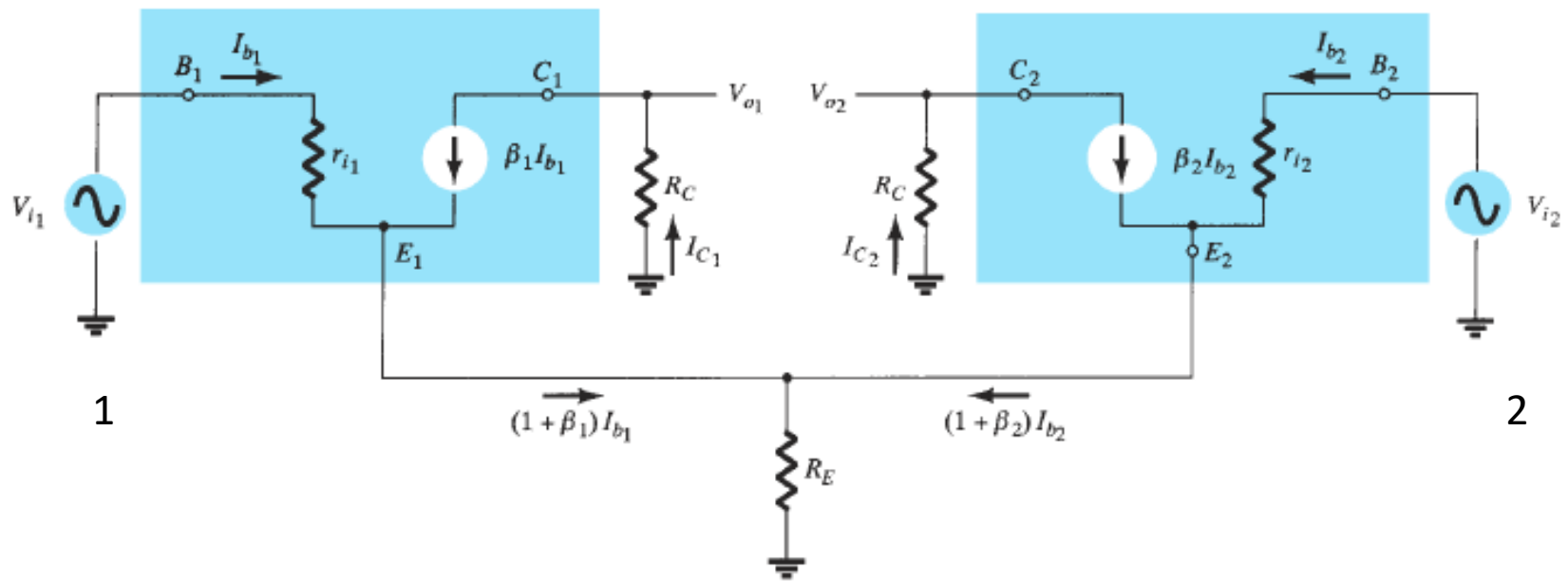
$$V_C = V_{CC} - I_C R_C = 9 \text{ V} - (1.25 \text{ mA})(3.9 \text{ k}\Omega) \approx 4.1 \text{ V}$$



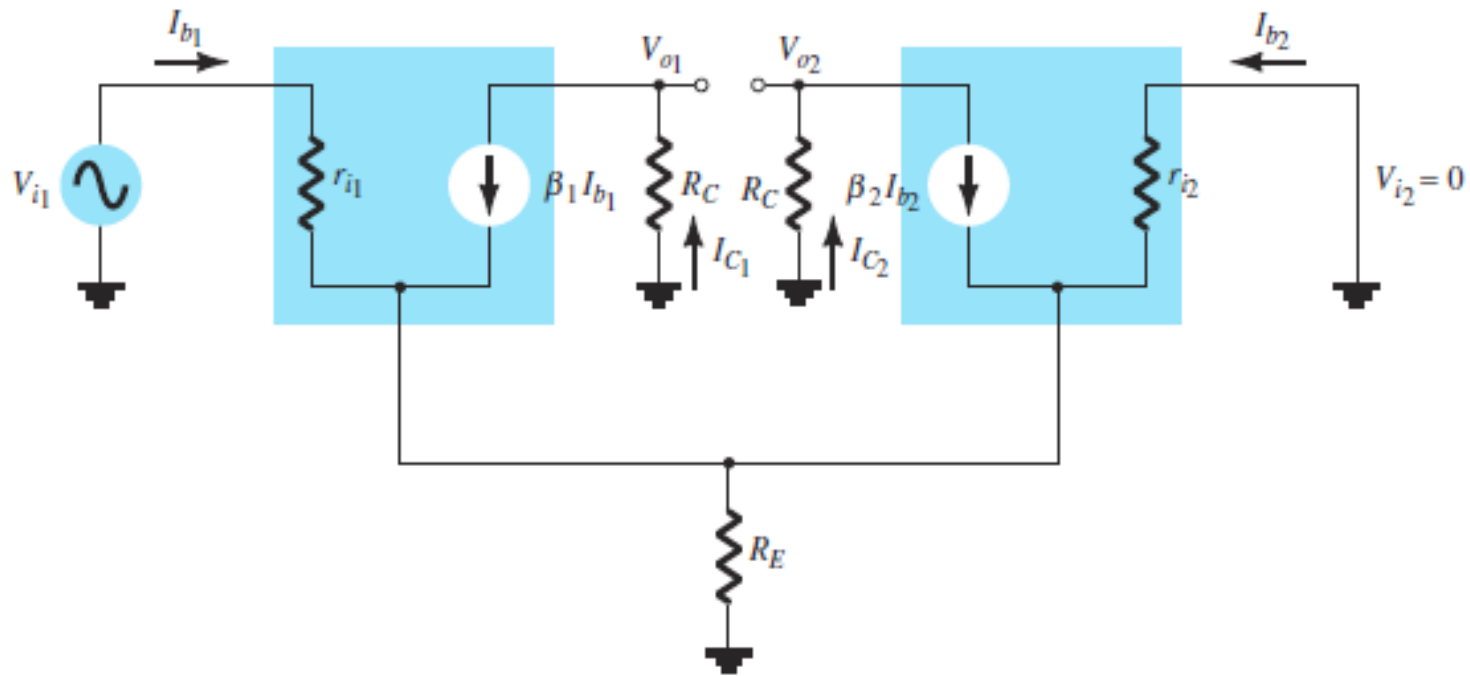

$$I_{b1} = -I_{b2} = I_b$$

$$r_{i1} = r_{i2} = r_i = \beta r_e$$

$$V_{i1} - I_b r_i - I_b r_i = 0$$

$$I_b = \frac{V_{i1}}{2r_i} = \frac{V_i}{2\beta r_e}$$

$$I_C = \beta I_b = \beta \frac{V_i}{2\beta r_e} = \frac{V_i}{2r_e}$$

$$r_e = V_t / I_E$$

$$V_o = - \frac{V_i}{2r_e} R_C = \frac{R_C}{2r_e} V_i$$

$$A_v = -R_C / 2r_e$$

$$A_v = -R_C / 2r_e$$


$$V_{o1} = -R_C / 2r_e v_{i1} + R_C / 2r_e v_{i2}$$

$$V_{o2} = R_C / 2r_e v_{i1} - R_C / 2r_e v_{i2}$$

$$v_i = v_{i1} - v_{i2}$$

$$V_o = v_{o1} - v_{o2} = -R_C / r_e (v_{i1} - v_{i2})$$

$$= -R_C / r_e v_d$$

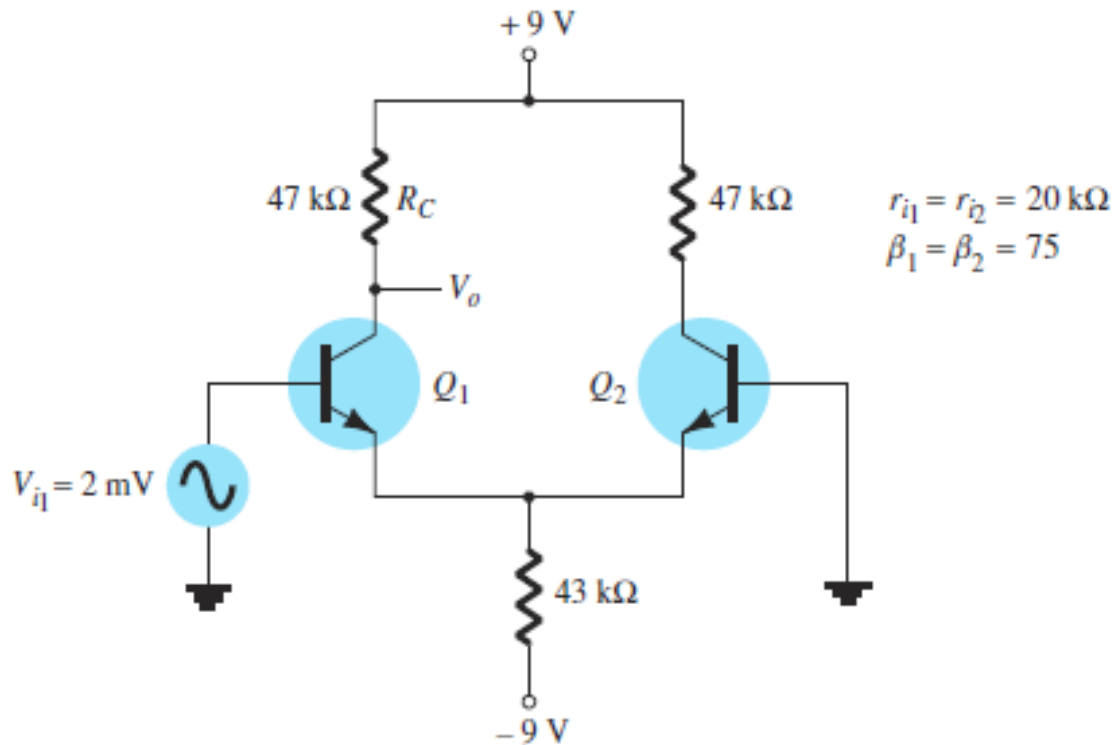

$$A_v = -47/2 * 0.267$$

$$= -88$$

$$V_o = -176 \text{ mV}$$

$$I_E = 8.3/43 \text{ mA}$$

$$r_e = 25 * 43 * 2 / 8.3 \text{ }\Omega = 269 \text{ }\Omega$$

$$R_e = 20/75 \text{ k}\Omega = 267 \text{ }\Omega$$

sayak mandal

2:22 PM

001910701014

Tandeep Singh

2:22 PM

001910701002

Abhishek Sarkar

2:22 PM

Abhishek Sarkar 001910701027

Sandip Dutta

2:22 PM

Sandip Dutta - 0019 1070 1017

Sagnik Banerjee

2:22 PM

001910701015

Snehasish Roy

2:22 PM

Snehasish Roy 001910701013

sagar sarkar

2:22 PM

0019107010141

Roudrini Mukherjee


2:22 PM


001910701053- Roudrini Mukherjee

ajoy dey

The properties associated with an ideal Amplifier are:

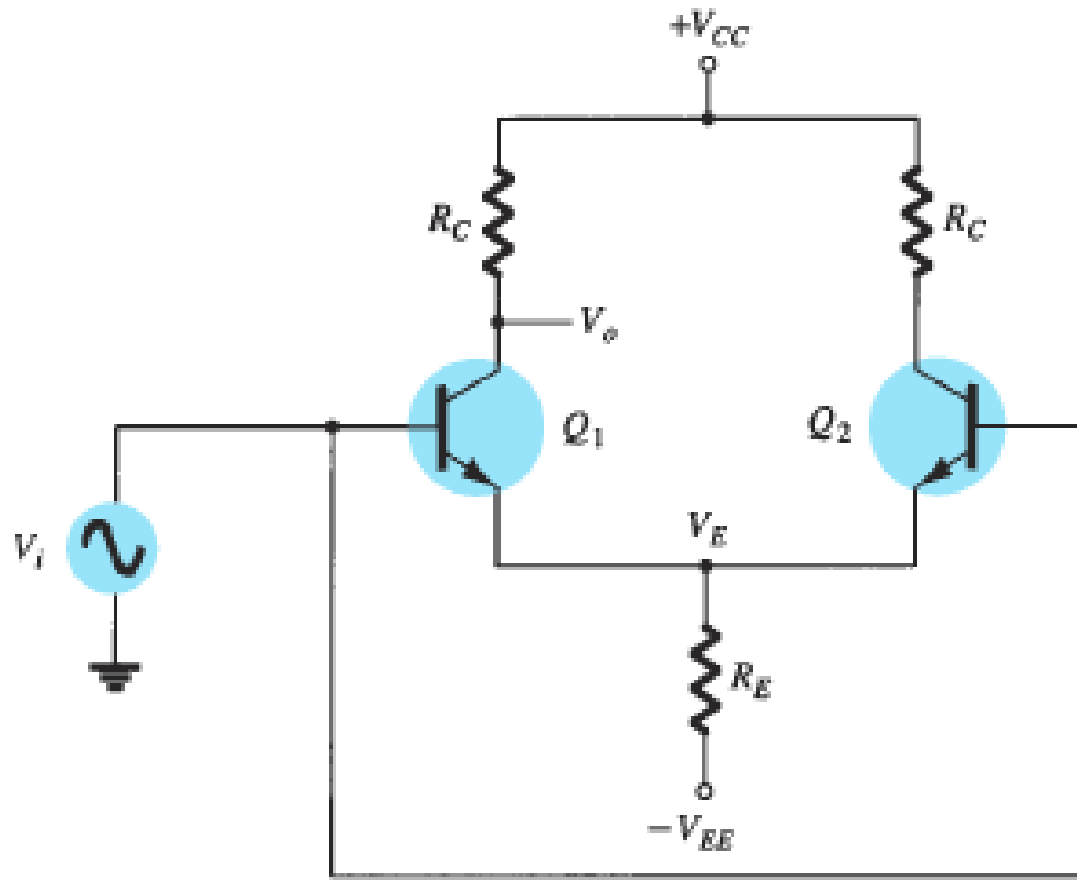1. infinite voltage gain (  $A_v \rightarrow \infty$  )
2. Infinite input impedance (  $Z_{in} \rightarrow \infty$  )
3. Zero output impedance(  $Z_{out} \rightarrow 0$  )
4. Output voltage  $V_{out} = 0$  when input voltages  $V_1 = V_2$
5. Infinite bandwidth ( no delay of the signal through the amplifier)



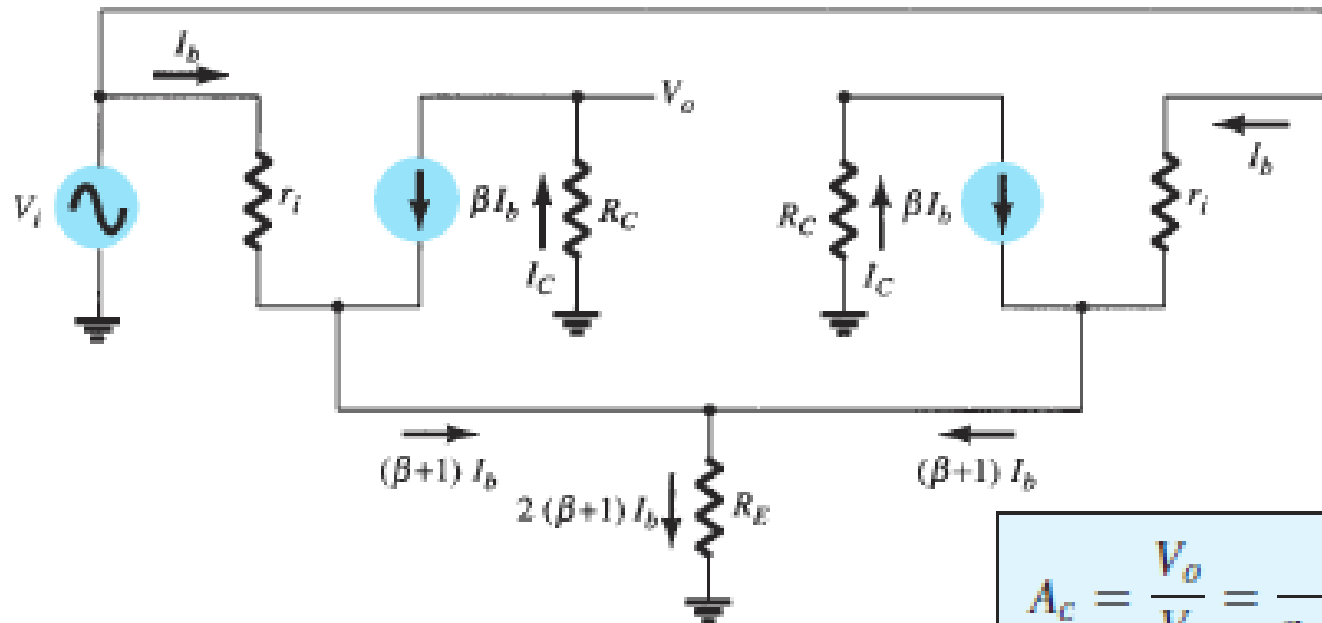

$$A_c = \frac{V_o}{V_i} = \frac{-\beta R_C}{r_i + 2(\beta + 1)R_E}$$

$$I_b = \frac{V_i}{r_i + 2(\beta + 1)R_E}$$

$$A_c = -R_C / (r_e + 2R_E)$$


$$V_o = -I_C R_C = \beta I_b R_C = \frac{-\beta V_i R_C}{r_i + 2(\beta + 1)R_E}$$


$\beta_1 \beta_2$

RC1 RC2

$A_{CM}=?$
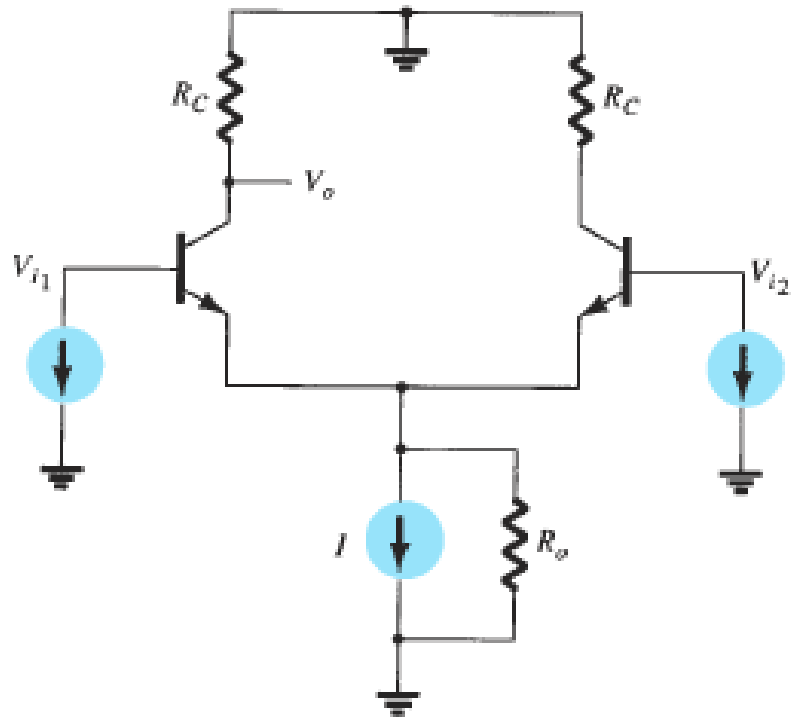
$$A_c = \frac{V_o}{V_i} = \frac{-\beta R_C}{r_i + 2(\beta + 1)R_E} = \frac{-75(47 \text{ k}\Omega)}{20 \text{ k}\Omega + 2(76)(43 \text{ k}\Omega)} = -0.54$$



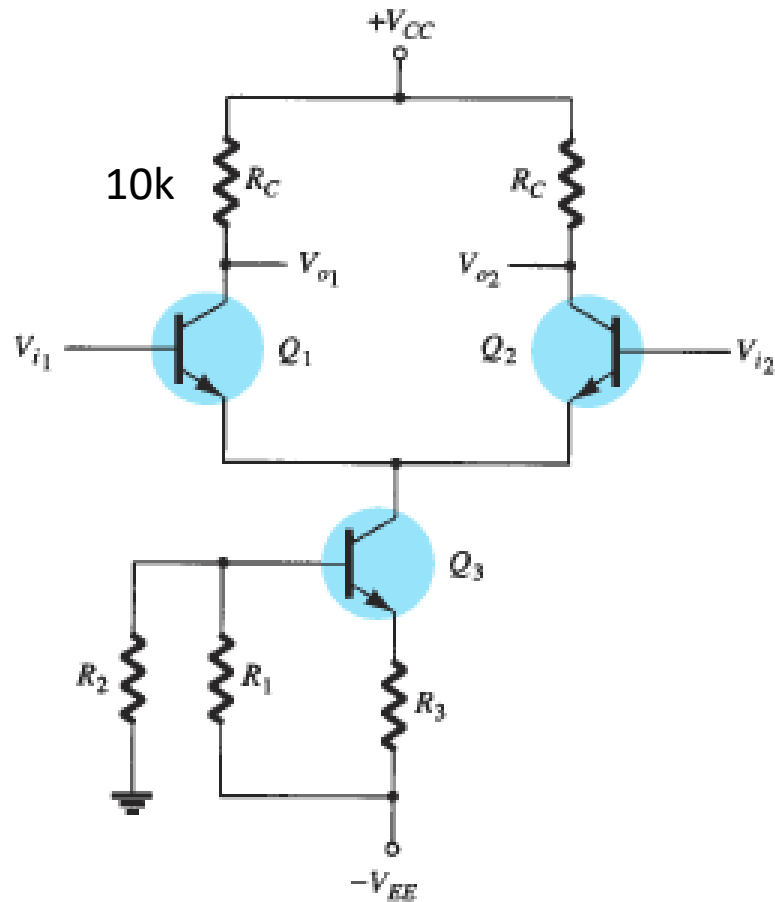

$R_2=1k$


$$\beta_1 = \beta_2 = \beta = 75$$

$$r_{i1} = r_{i2} = r_i = 11 \text{ k}\Omega$$

$$Q_3$$

$$r_o = 200 \text{ k}\Omega$$

$$\beta_3 = 75$$

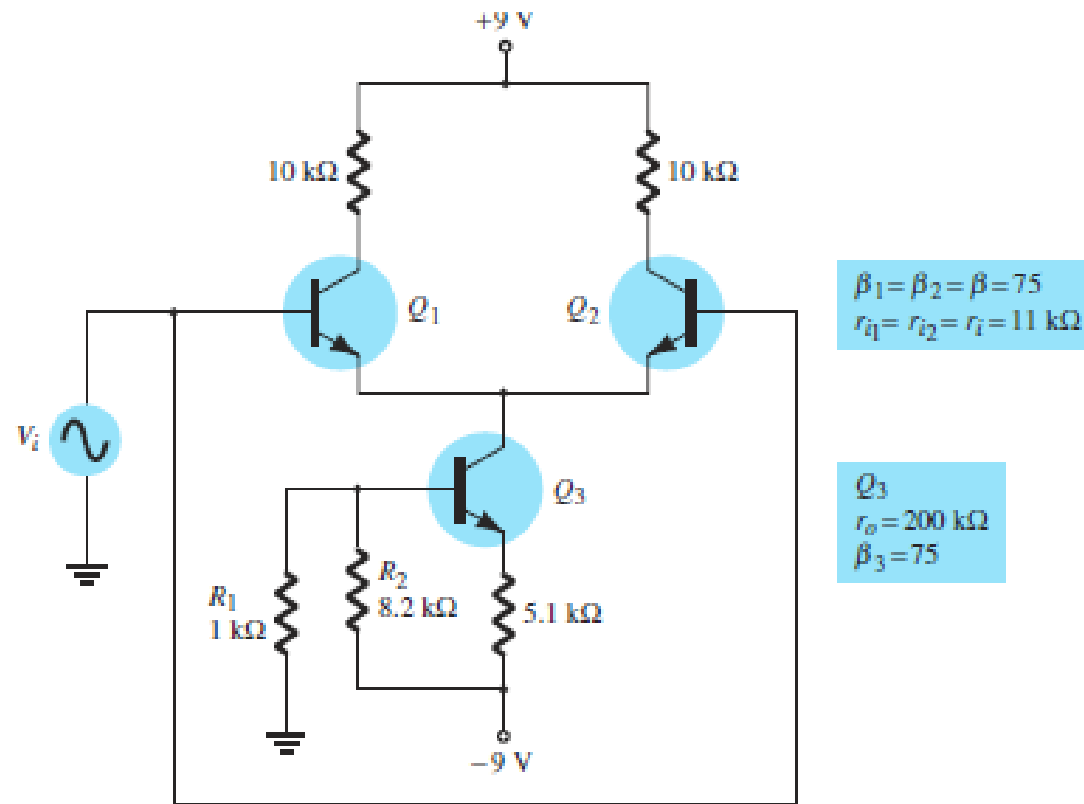


$$A_c = \frac{\beta R_C}{r_i + 2(\beta + 1)R_E} = \frac{75(10 \text{ k}\Omega)}{11 \text{ k}\Omega + 2(76)(200 \text{ k}\Omega)} = 24.7 \times 10^{-3}$$



Closed-loop

## The inverting configuration

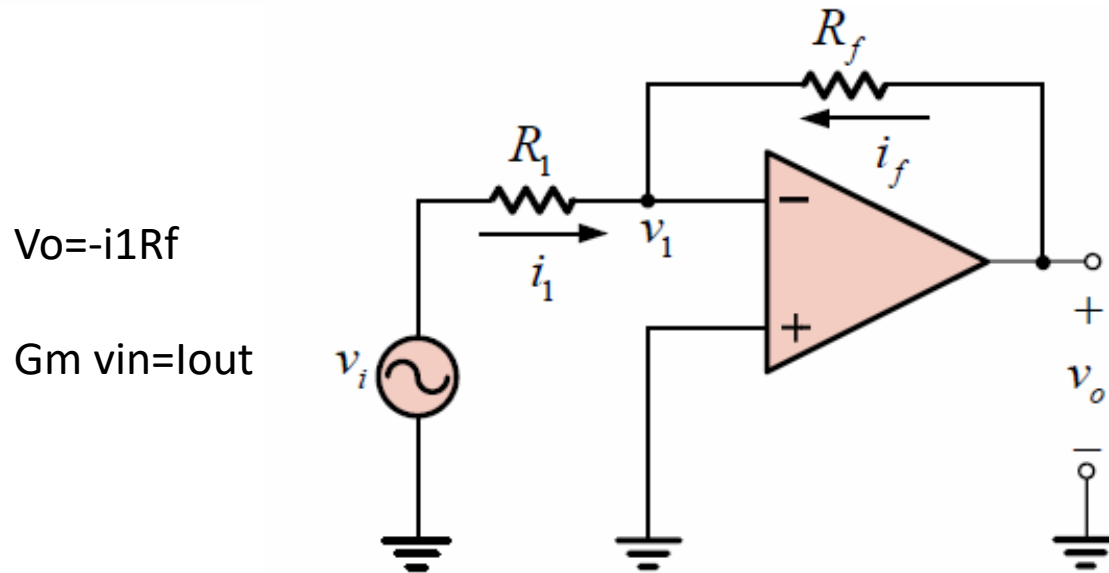

$$V_o = -i_1 R_f$$

$$G_m v_{in} = I_{out}$$

$$v_d = v_1$$

$$A_d = \infty$$

$$V_o = -A_d(v_1 - v_2)$$

$$(v_1 - v_2) = -v_o / A_d = 0$$

$$v_1 = v_2 = 0$$

Virtual short

Virtual ground

$$I_i = 0, R_{in} = \infty$$

$$i_1 = \frac{v_i - v_1}{R_1} = \frac{v_i - 0}{R_1} = \frac{v_i}{R_1}$$


$$v_o = v_1 + i_f R_f = v_1 - i_1 R_f$$

$$A_v = -R_f / R_1$$

$$i_1 = \frac{v_i - \left(-\frac{v_o}{A}\right)}{R_1} = \frac{v_i + \left(\frac{v_o}{A}\right)}{R_1}$$

$$v_o = -\frac{v_o}{A} - i_1 R_f$$
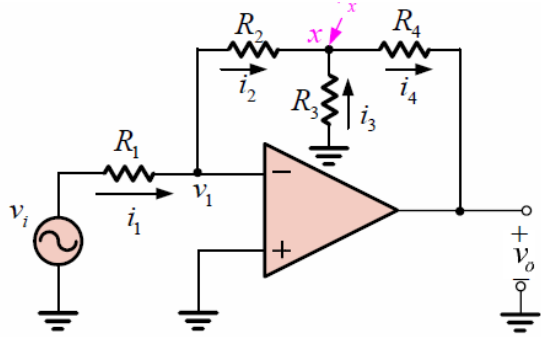
$$\frac{v_o}{v_i} = \frac{-R_f / R_1}{1 + (1 + R_f / R_1) / A}$$



$$v_x = v_1 - i_2 R_2 = 0 - \left( \frac{v_i R_2}{R_1} \right)$$

$$= -v_i R_2 / R_1$$

$$i_3 = \frac{0 - v_x}{R_3} = \frac{R_2}{R_1 R_3} v_i$$

$$i_4 = i_2 + i_3 = \frac{v_i}{R_1} + \frac{R_2}{R_1 R_3} v_i$$

$$v_o = v_x - i_4 R_4$$

$$= -\frac{v_i}{R_1} R_2 - \left( \frac{v_i}{R_1} + \frac{R_2}{R_1 R_3} v_i \right) R_4$$

$$\frac{v_o}{v_i} = -\frac{R_2}{R_1} \left( 1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right)$$

$$v_x = v_1 - i_2 R_2 = 0 - \left( \frac{v_i R_2}{R_1} \right)$$

$$= -v_i R_2 / R_1$$


$$i_3 = \frac{0 - v_x}{R_3} = \frac{R_2}{R_1 R_3} v_i$$

$$i_4 = i_2 + i_3 = \frac{v_i}{R_1} + \frac{R_2}{R_1 R_3} v_i$$

$$v_0 = v_x - i_4 R_4$$

$$= -\frac{v_i}{R_1} R_2 - \left( \frac{v_i}{R_1} + \frac{R_2}{R_1 R_3} v_i \right) R_4$$

## The Weighted Summer

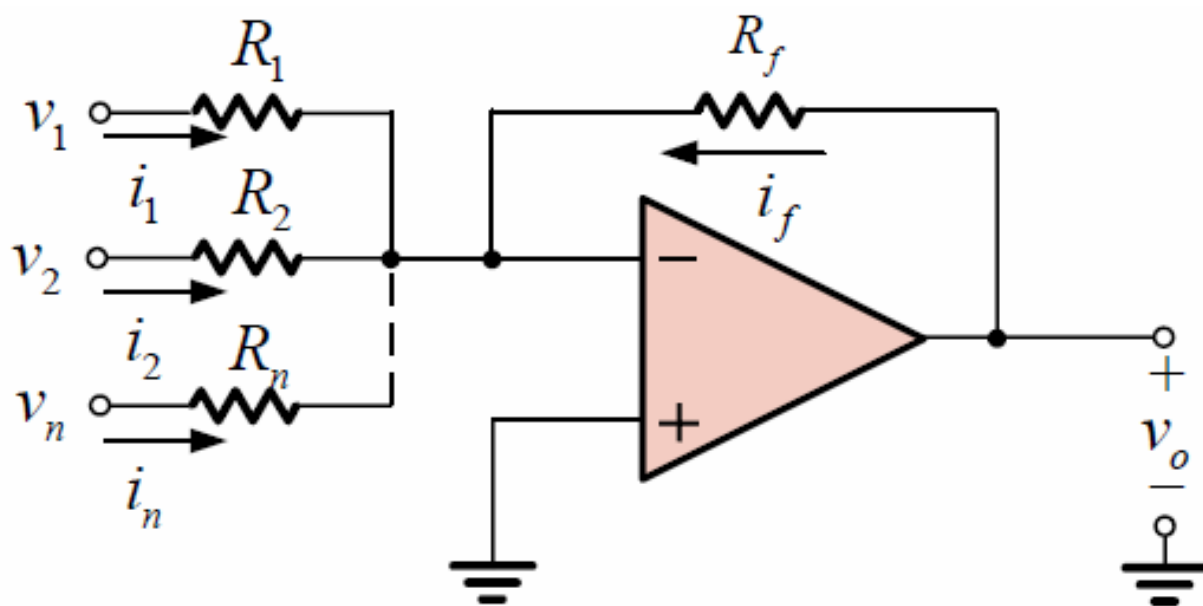


$$i_1 = \frac{v_1}{R_1}, i_2 = \frac{v_2}{R_2}, I_n = \frac{v_n}{R_n}, \quad I_f = \frac{v_o}{R_f}$$


$$I_f = -(I_1 + I_2 + \dots + I_n) \quad \Rightarrow \quad \frac{v_o}{R_f} = -\left(\frac{v_1}{R_1} + \frac{v_2}{R_2} + \dots + \frac{v_n}{R_n}\right)$$

$$R_1 = R_2 = \dots = R_n = R_f \quad \text{Then } v_o = -(v_1 + v_2 + \dots + v_n)$$

# Integrators and Differentiators

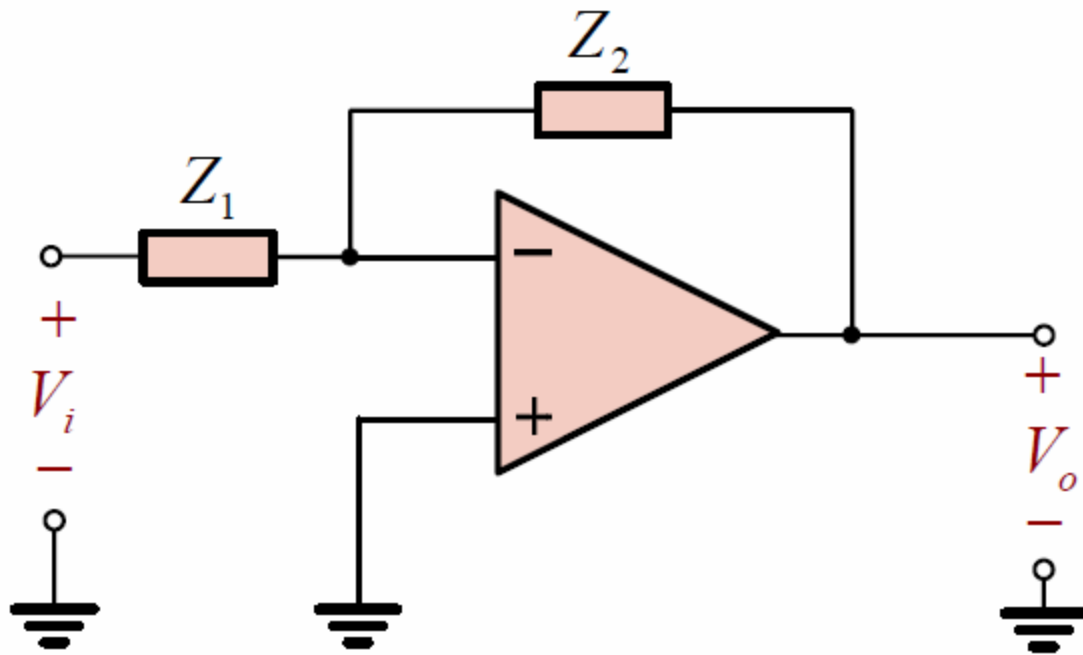

$$\frac{V_o}{V_i} = -\frac{Z_2}{Z_1}$$

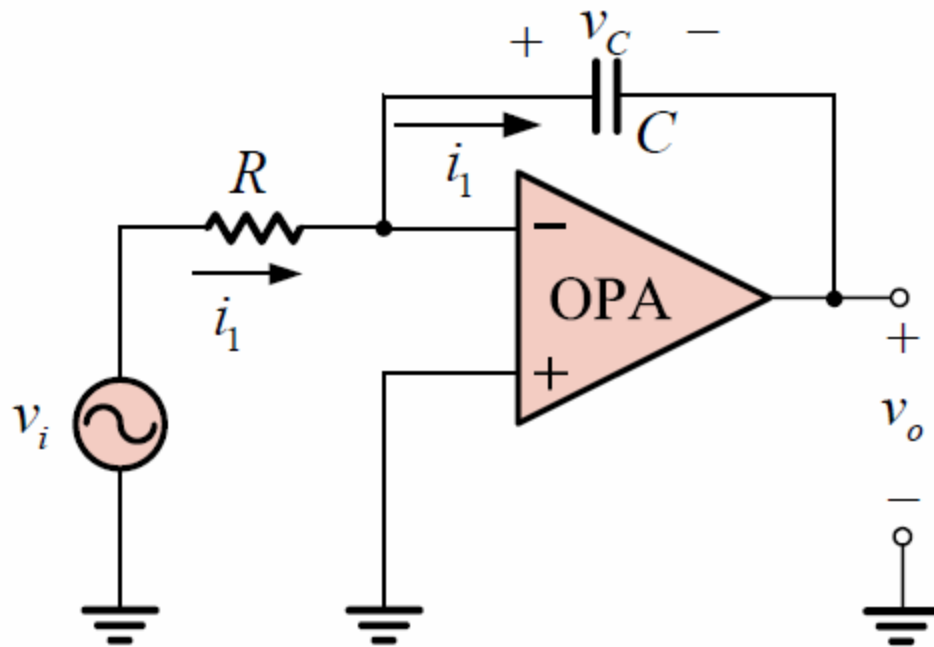

$$v_c(t) = V_c + \frac{1}{C} \int_0^t i_1(t) dt$$

$$v_o(t) = -v_c(t) = -V_c - \frac{1}{C} \int_0^t i_1(t) dt = -V_c - \frac{1}{RC} \int_0^t v_i(t) dt$$

$$s=j\omega$$


$$\frac{v_o(s)}{v_1(s)} = -\frac{1}{sRC}$$


$$\Rightarrow \frac{v_o(j\omega)}{v_1(j\omega)} = -\frac{1}{j\omega RC}$$

$$\left| \frac{v_o}{v_1} \right| = \frac{1}{\omega RC} = \frac{\omega_t}{\omega}, \quad \angle v_o / v_1 = +90^\circ$$

The unity gain frequency  $\omega_t$  as


$$\omega_t = \frac{1}{RC}$$

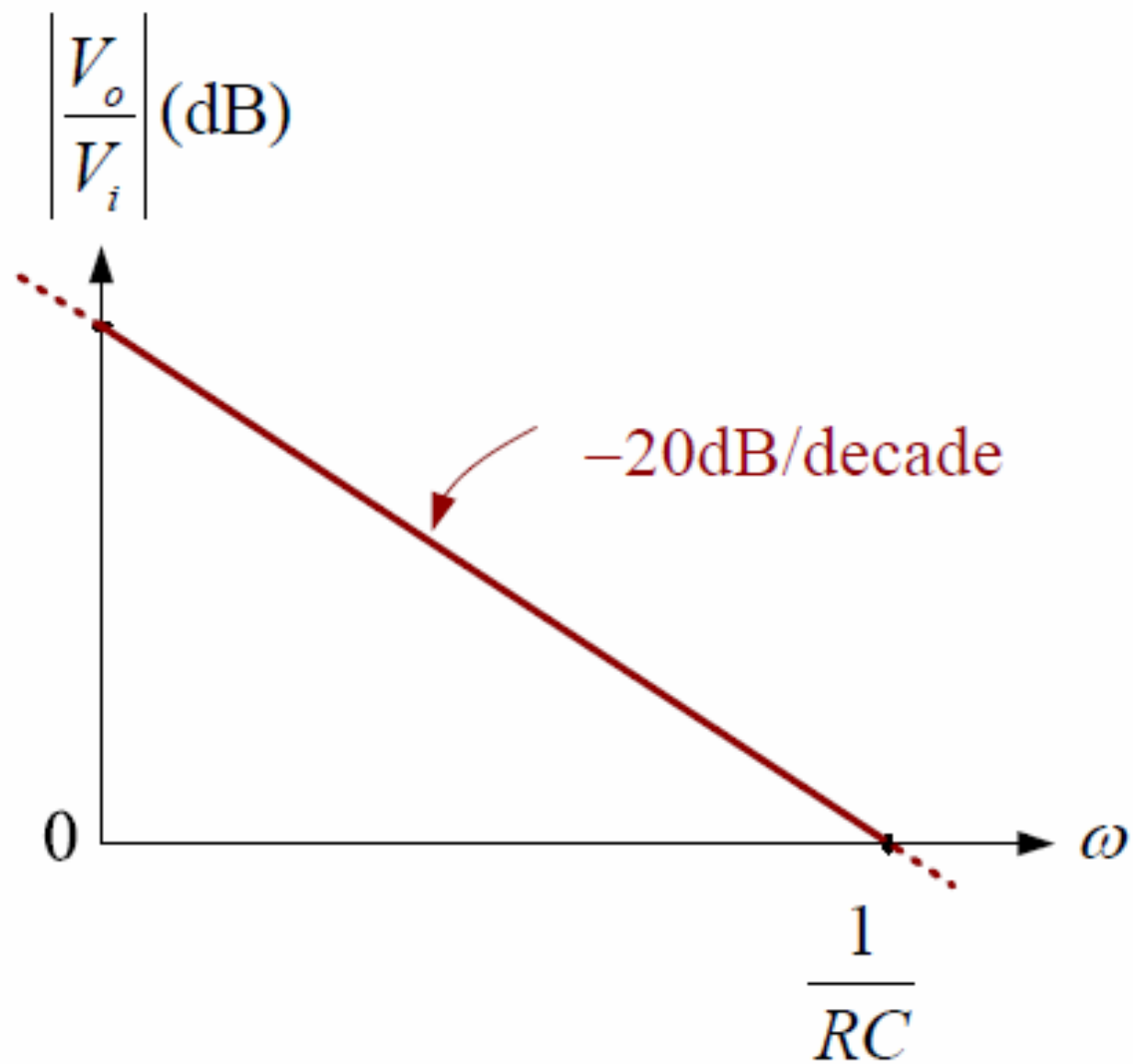

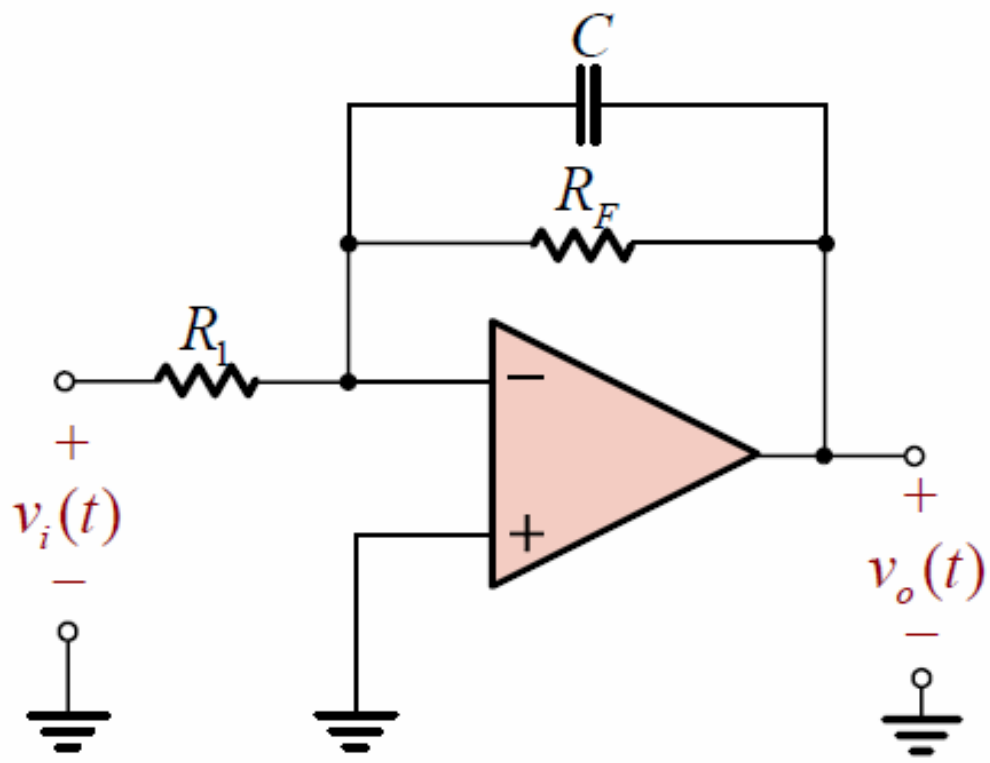

$$\frac{v_o(s)}{v_1(s)} = -\frac{\frac{R_F}{1 + sR_F C}}{R} = -\frac{R_F / R}{1 + sR_F C}$$


## The Op-Amp Differentiator

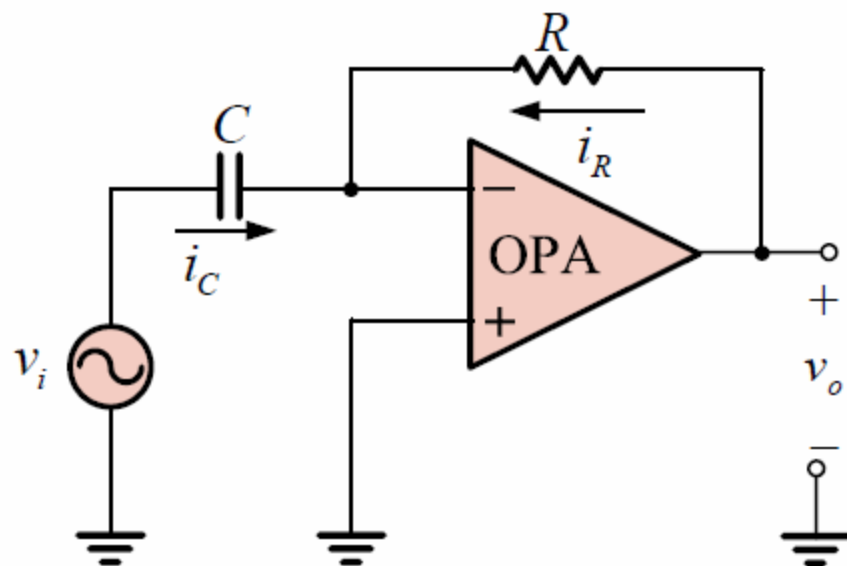

$$Q = Cv_i, \quad i_c = \frac{dQ}{dt} \Rightarrow i_c = C \frac{dv_i}{dt}, \quad I_R = \frac{v_o}{R}$$


$$-i_R = i_c \Rightarrow C \frac{dv_i}{dt} = -\frac{v_o}{R} \Rightarrow v_o = -RC \frac{dv_i}{dt}$$
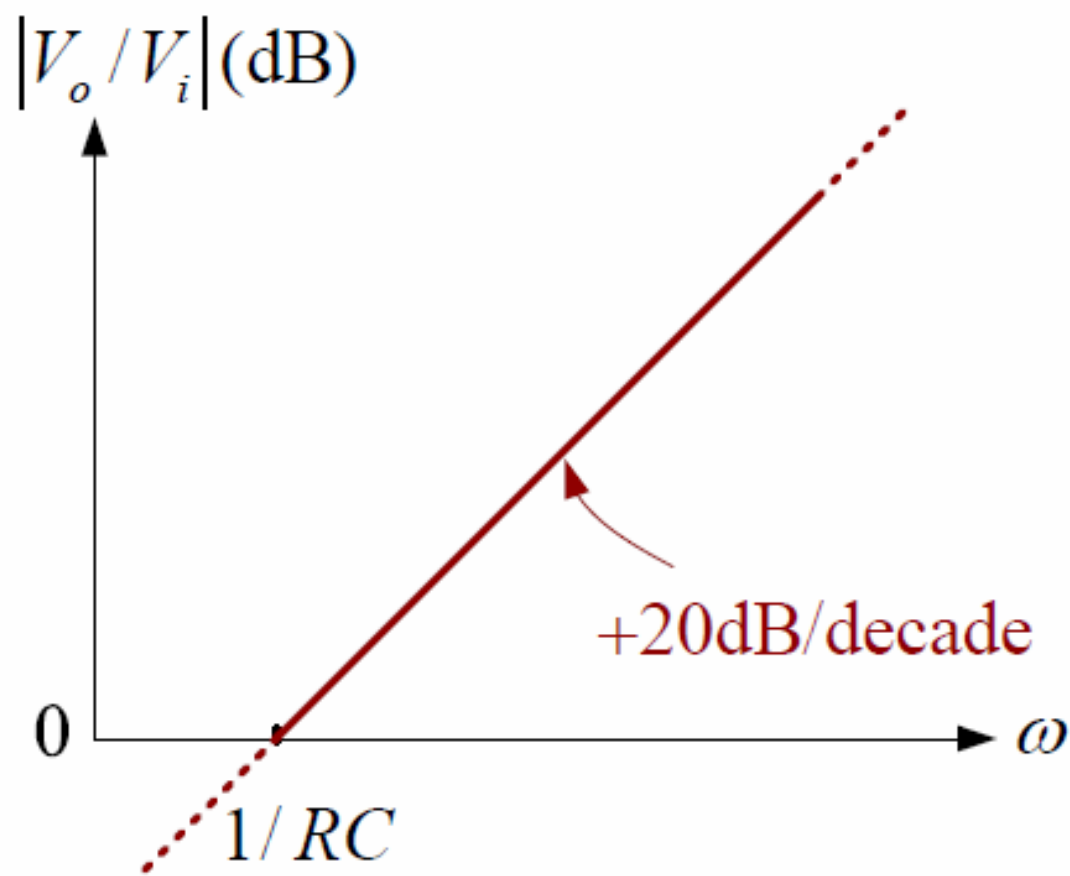
$$\frac{v_o(s)}{v_1(s)} = -sRC \Rightarrow \frac{v_o(j\omega)}{v_1(j\omega)} = -j\omega RC$$



$$\left| \frac{v_o}{v_1} \right| = \omega RC = \frac{\omega}{\omega_t}$$

# Noninverting Configuration

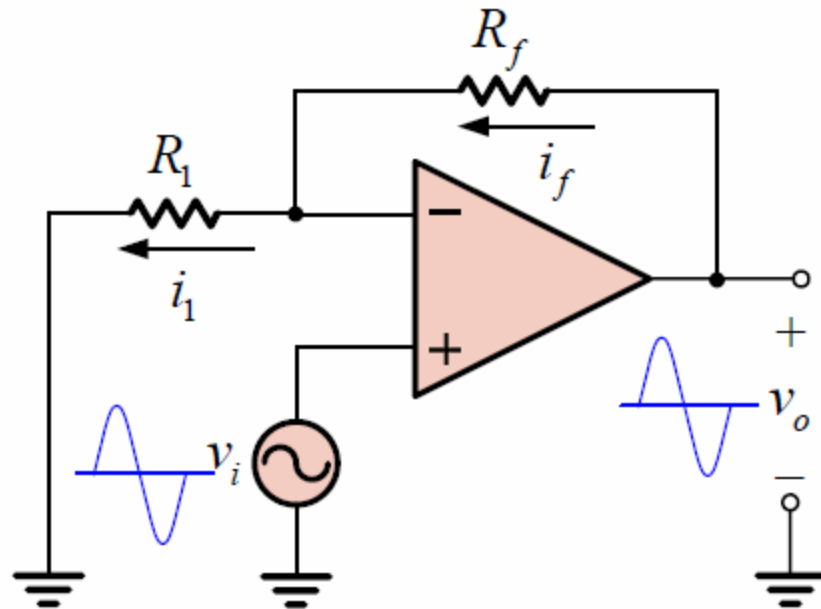

$$i_1 = \frac{v_i}{R_1}, \quad i_f = \frac{v_o - v_i}{R_f}$$

$$i_1 = i_f \Rightarrow \frac{v_i}{R_1} = \frac{v_o - v_i}{R_f} \quad \Rightarrow v_o = \left(1 + \frac{R_f}{R_1}\right)v_i$$

$$v_- = v_i - (v_o / A)$$


$$i_1 = \frac{v_i - (v_o / A)}{R_1}, i_f = \frac{v_o - [v_i - (v_o / A)]}{R_f} = \frac{v_o - v_i + (v_o / A)}{R_f},$$


$$i_1 = i_f \Rightarrow \frac{v_i - (v_o / A)}{R_1} = \frac{v_o - v_i + (v_o / A)}{R_f}$$

$$v_i A (R_1 + R_f) = v_o [(1 + A)R_1 + R_f]$$

$$\frac{v_o}{v_i} = \frac{1 + (R_f / R_1)}{1 + \frac{1 + (R_f / R_1)}{A}}$$

# Voltage Follower

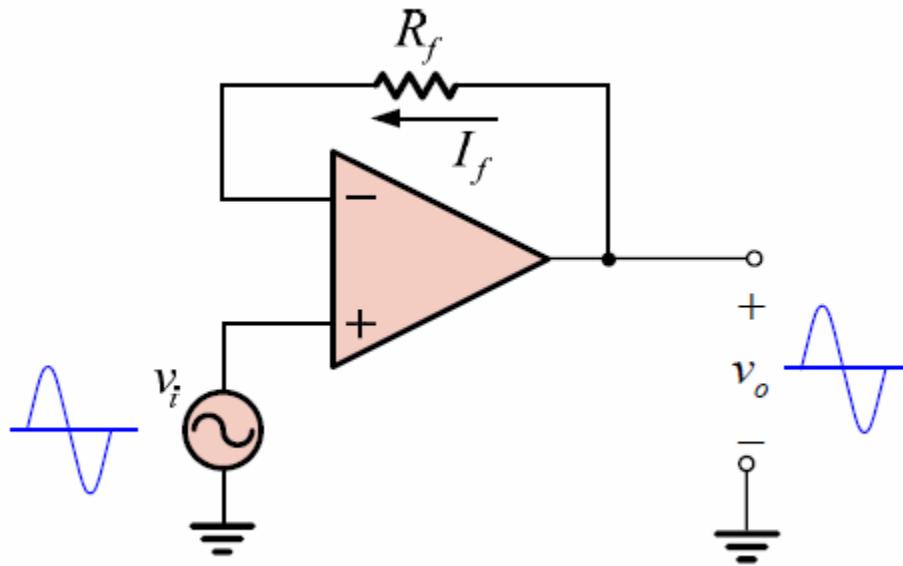

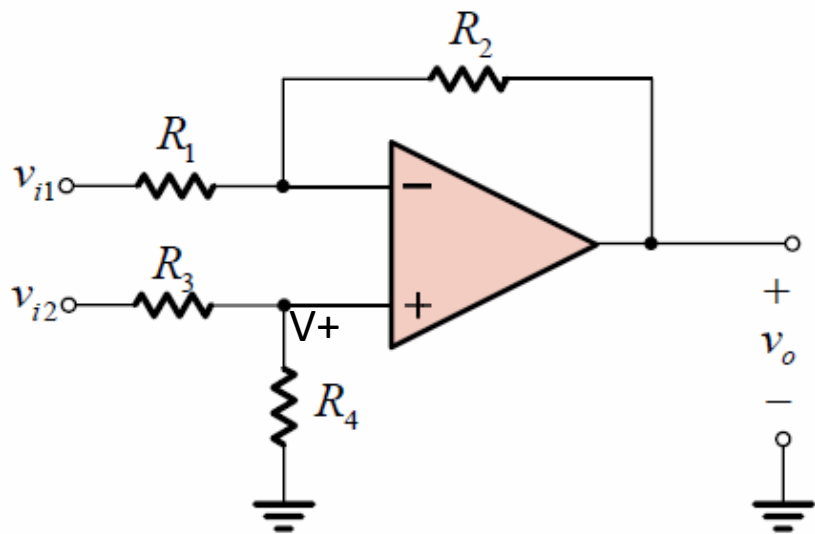

(1) Assume  $v_{i1} = 0$ ,

$$\begin{aligned} \text{then } v_o' &= v_+ \left( 1 + \frac{R_2}{R_1} \right) \\ &= \frac{R_4}{R_3 + R_4} v_{i2} \left( 1 + \frac{R_2}{R_1} \right) \end{aligned}$$

(2) Assume  $v_{i2} = 0$ ,

$$\text{then } v_o'' = v_{i1} \left( -\frac{R_2}{R_1} \right)$$

$$\begin{aligned} v_o &= v_o' + v_o'' \\ &= \frac{R_4}{R_3 + R_4} v_{i2} \left( 1 + \frac{R_2}{R_1} \right) + v_{i1} \left( -\frac{R_2}{R_1} \right) \end{aligned}$$

If  $R_1 = R_3 = R_a$ ,  $R_2 = R_4 = R_b$

$$\text{then } v_o = \frac{R_b}{R_a} (v_{i2} - v_{i1}) = \frac{R_b}{R_a} v_{id}$$

$$A_d = \frac{R_b}{R_a} \quad (2.17)$$

001910701020

Keshav Jasrotia

2:17 PM

001910701003

Souvik Das

2:17 PM

001910701010 Souvik Das

MAINAK MONDAL

2:17 PM

001910701016

ajoy dey

2:17 PM

001910701068

Gaurav Nandy

2:17 PM

001910701074-Gaurav Nandy

Arijit Saha

2:17 PM

001910701019

Sagnik Das

2:17 PM

Sagnik Das 001910701075

Debadri Sengupta


2:18 PM



001910701045 Debadri Sengupta

Sanjoy Maico


# DC Imperfections


i/o Offset Voltage

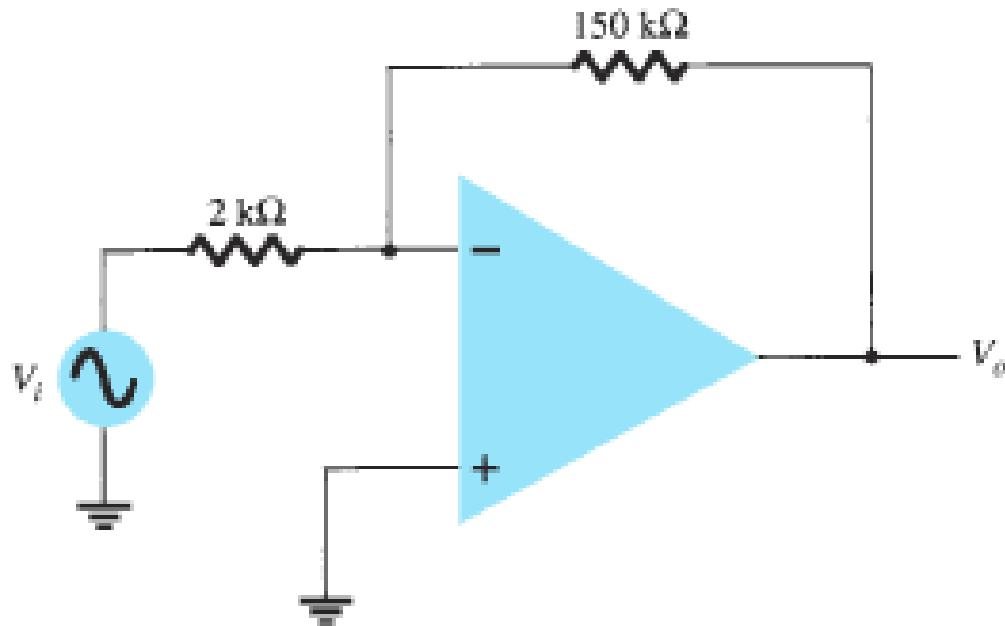

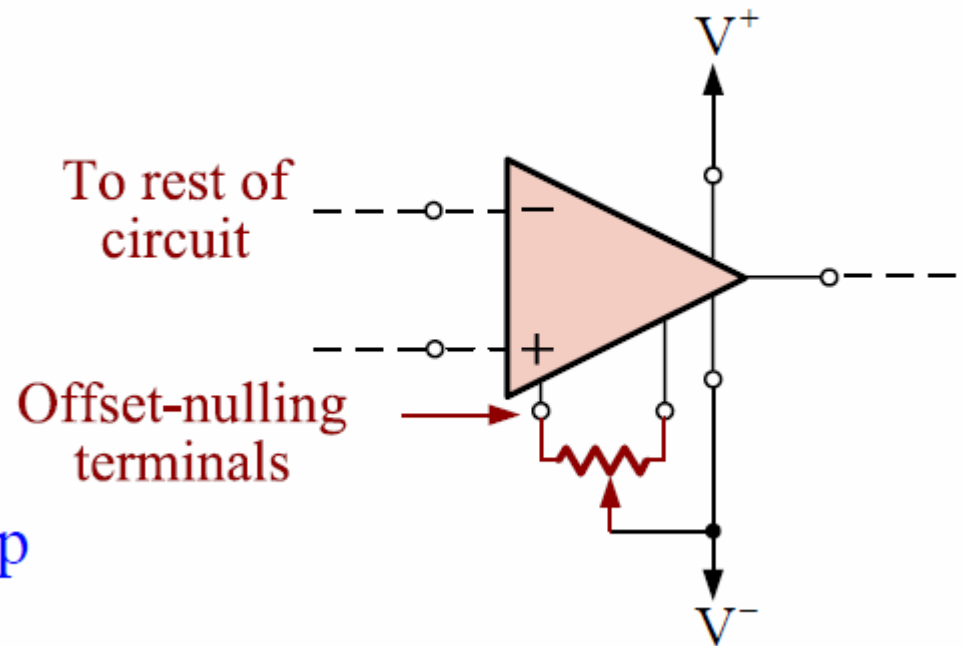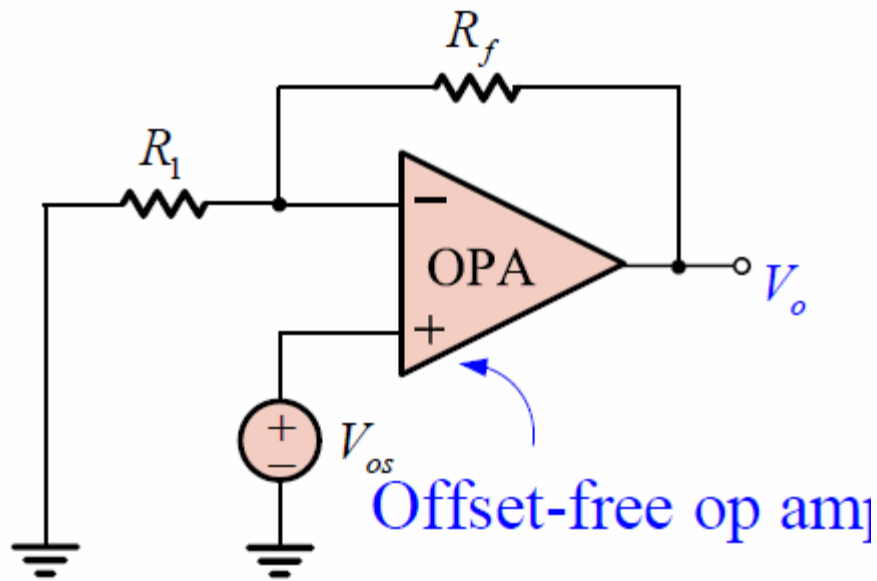

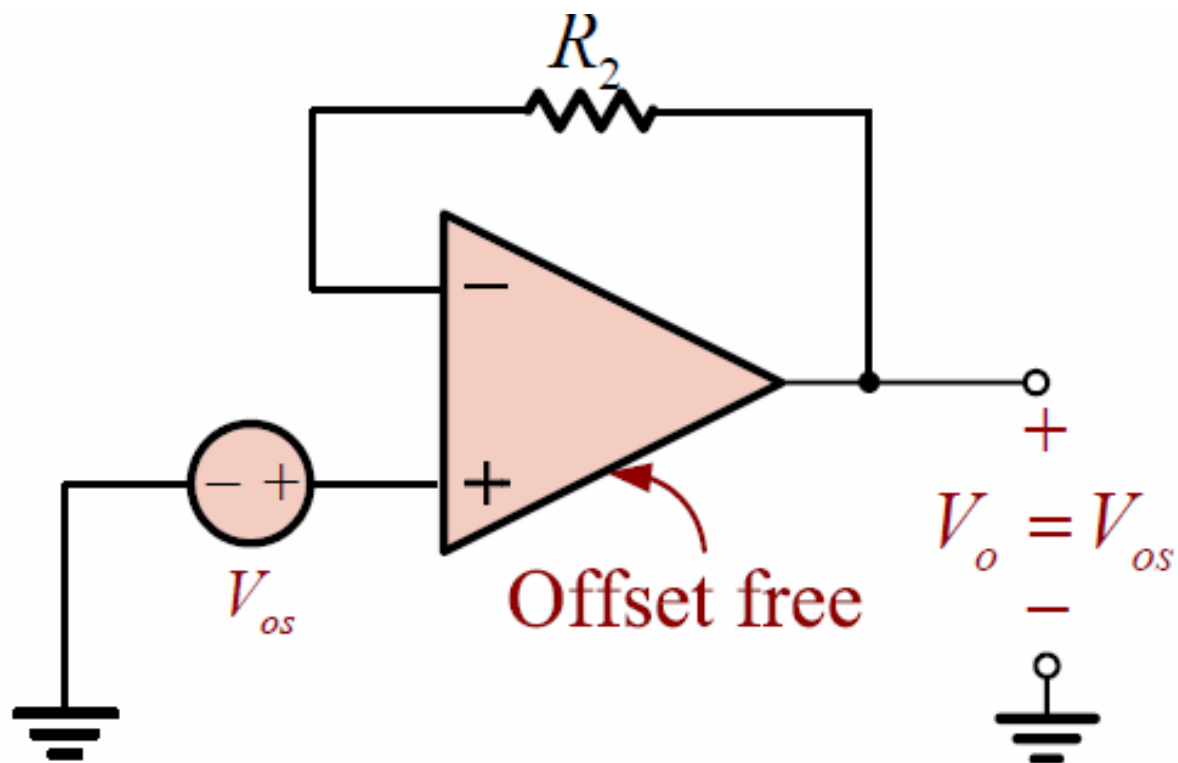
$$V_o = V_{os} \left( 1 + \frac{R_2}{R_1} \right)$$



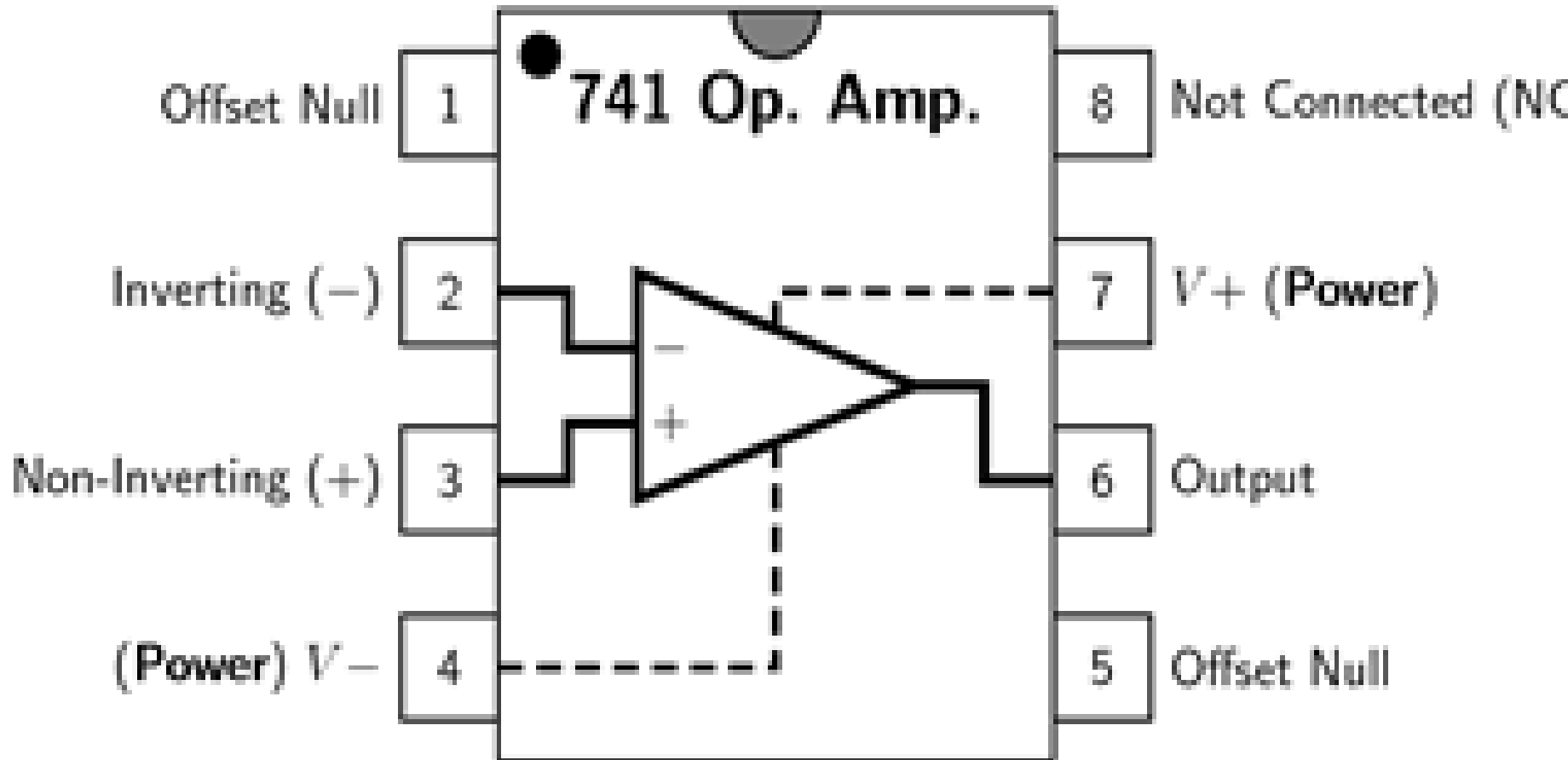


Input bias current

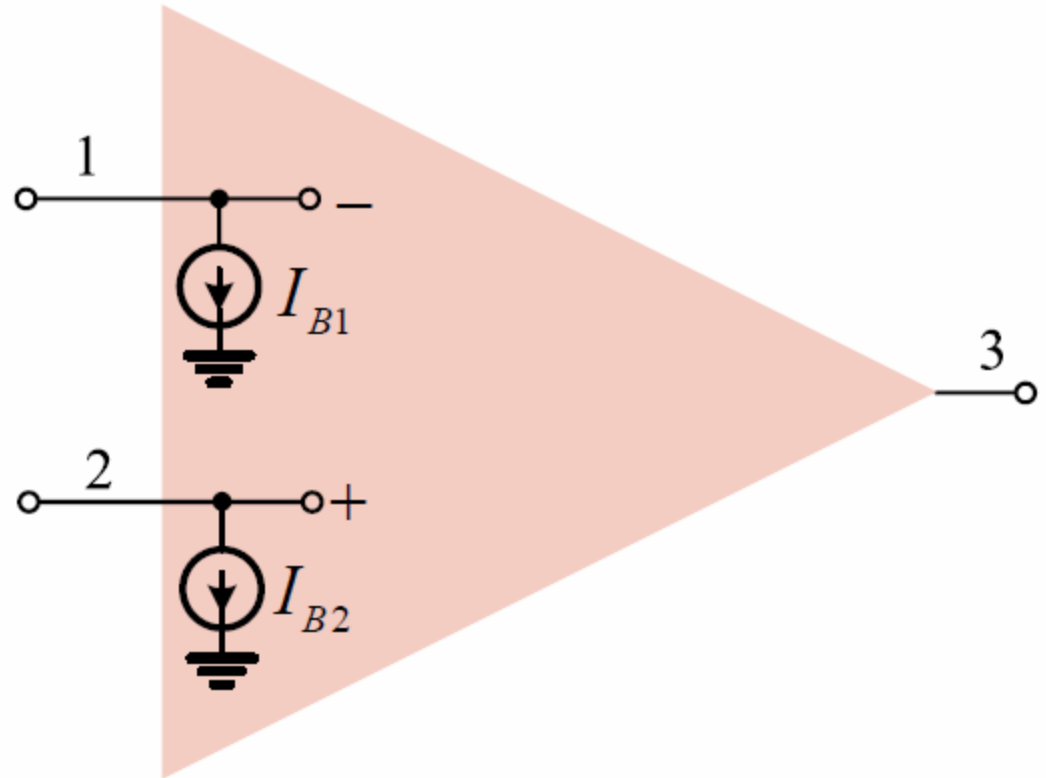


$$I_B = \frac{I_{B1} + I_{B2}}{2}$$

Offset current

$$I_{OS} = |I_{B1} - I_{B2}|$$

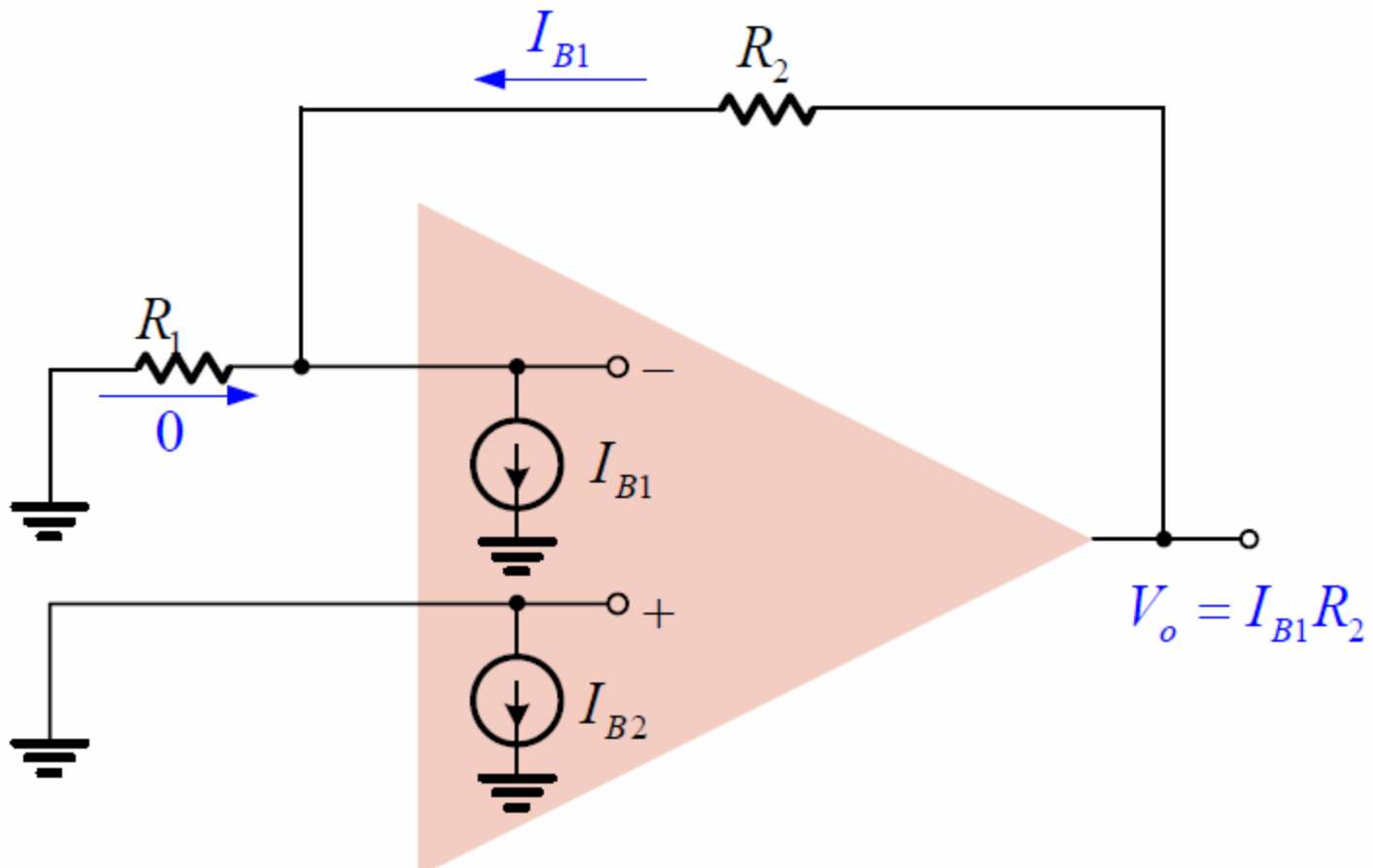

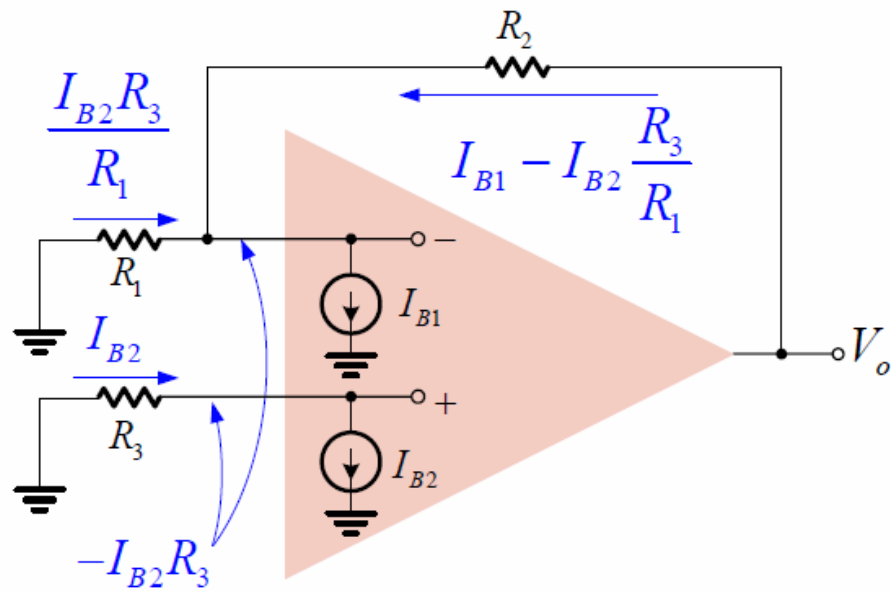

$$V_o = -I_{B2}R_3 + R_2 \left( I_{B1} - I_{B2}R_3 / R_1 \right)$$

Consider first case  $I_B = I_{B1} = I_{B2}$ , which results in

$$V_o = I_B \left[ R_2 - R_3 \left( 1 + R_2 / R_1 \right) \right]$$


Thus we can reduce  $V_o$  to zero by selecting  $R_3$  such that

$$R_3 = \frac{R_2}{\left( 1 + R_2 / R_1 \right)} = \frac{R_1 R_2}{R_1 + R_2} = R_1 // R_2$$

# Effect of Finite Open-Loop Gain and Bandwidth on Circuit Performance

Unity gain bandwidth

$$f_1 = A_{VD} f_C$$

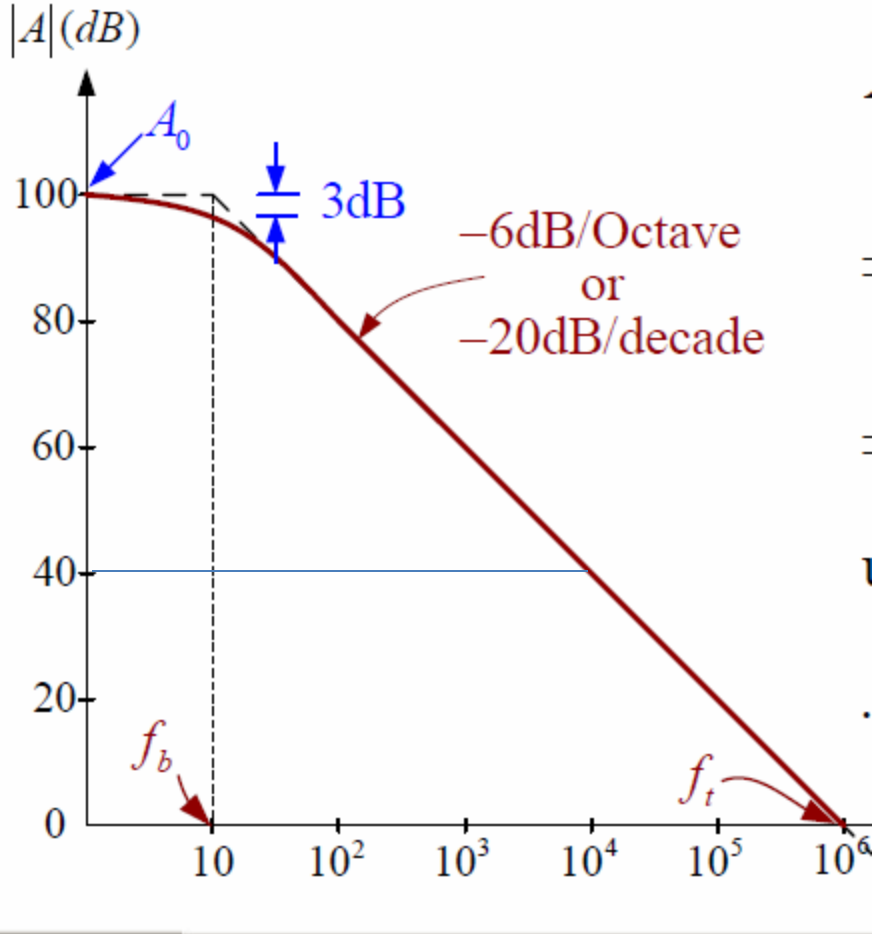

$$A(s) = \frac{A_0}{1 + (s / \omega_b)} = \frac{A_0}{1 + (j\omega / \omega_b)}$$

$$\Rightarrow A(j\omega) \approx \frac{A_0 \omega_b}{j\omega}$$

$$\Rightarrow |A(j\omega)| = \frac{A_0 \omega_b}{\omega}$$

unity gain frequency  $\omega_t = A_0 \omega_b$

$$\therefore A(j\omega) = \frac{\omega_t}{j\omega} \Rightarrow |A(j\omega)| = \frac{\omega_t}{\omega} = \frac{f_t}{f}$$

Slew rate

Slew rate = maximum rate at which amplifier output can change in volts per microsecond ( $V/\mu s$ )

$$SR = \frac{\Delta V_o}{\Delta t} \text{ V}/\mu s \quad \text{with } t \text{ in } \mu s$$

## Maximum Signal Frequency


$$2\pi fK \leq SR$$

$$\omega K \leq SR$$

$$f \leq \frac{SR}{2\pi K} \quad \text{Hz}$$

$$\omega \leq \frac{SR}{K} \quad \text{rad/s}$$
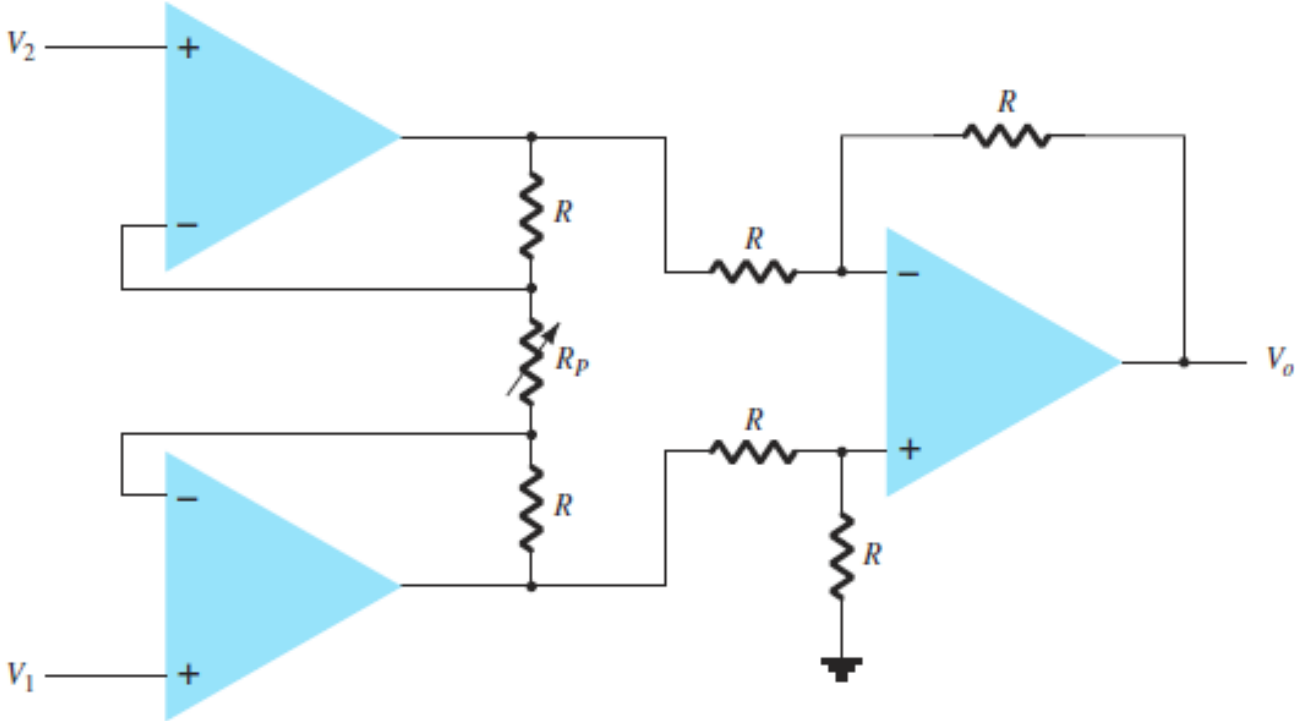
# A Superior Circuit: The Instrumentation Amplifier



001910701014

Abhijit Deogharia

6:34 PM

001910701024

Ayan Biswas

6:34 PM

001910701012 - AYAN BISWAS

arindam majee

6:34 PM

001910701006

Arijit Saha

6:34 PM

001910701019

Sarit Roy Chaudhury

6:34 PM

001910701096

sagar sarkar

6:34 PM

001910701041

Shubham singh

6:34 PM

001910701008

Snehasish Roy

6:34 PM

Snehasish Roy 001910701013

Asini Prayoon Das

# OP-AMPS WITH NEGATIVE FEEDBACK

- An op-amp can be connected using negative feedback to stabilize the gain and increase frequency response.
- The closed-loop voltage gain is the voltage gain of an op-amp with external feedback.
- The closed-loop voltage gain is determined by the external component values and can be precisely controlled by them.


# Op-Amp Parameters (4)

## Slew Rate


- The maximum rate of change of the output voltage in response to a step input voltage is the slew rate of an op-amp.
- The slew rate is dependent upon the high-frequency response of the amplifier stages within the op-amp.

$$\text{Slew rate} = \frac{\Delta V_{out}}{\Delta t}$$

- **Slew-rate measurement**

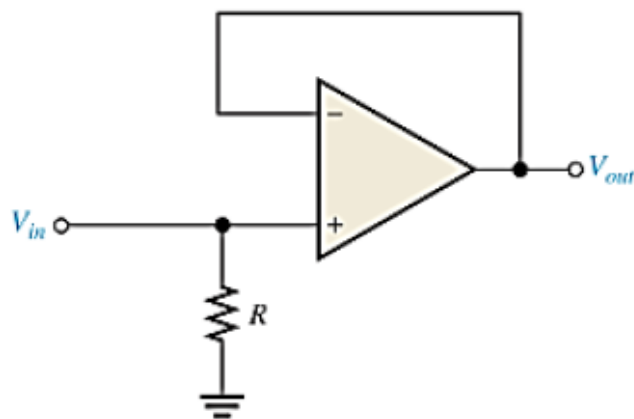

(a) Test circuit

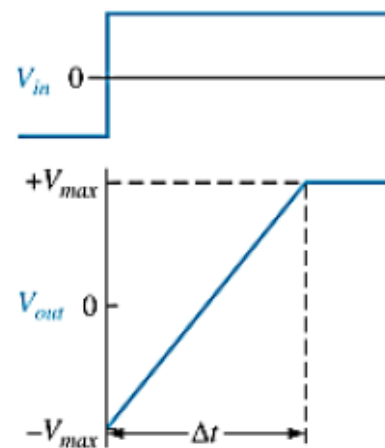

(b) Step input voltage and the resulting output voltage

## INSTRUMENTATION AMPLIFIERS

- Instrumentation amplifiers are commonly used in environments with high common-mode noise such as in data acquisition systems where remote sensing of input variables is required.
- The main purpose of an instrumentation amplifier is to amplify small signals that may be riding on large common-mode voltages.
- The key characteristics are high input impedance, high common-mode rejection, low output offset, and low output impedance.

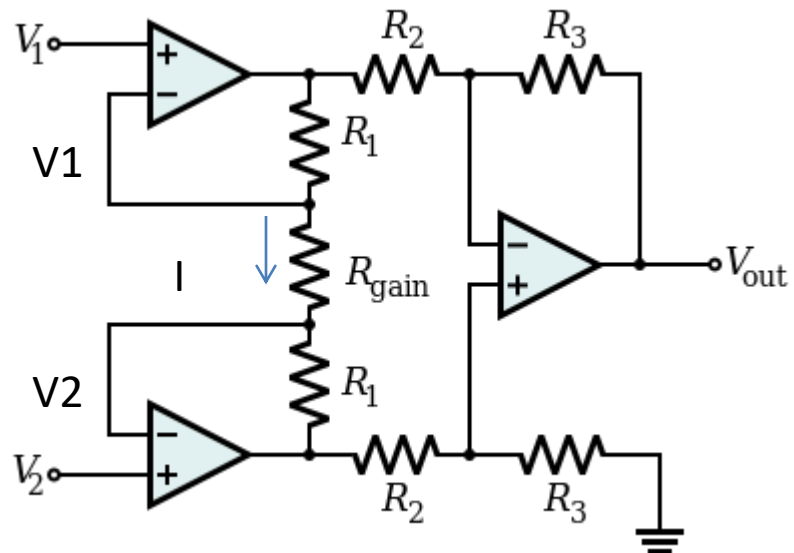


Fig. The basic instrumentation amplifier using three op-amps.

$$I = (V_{o1}-V_{o2})/(R_1+R_{gain}+R_1) \dots\dots\dots(1)$$

$$I = (V_{o1}-V_{o2})/(2R_1+R_{gain})$$

Since no current is flowing to the input of the op-amps 1 & 2, the current I between the nodes G and H can be given as,

$$I = (V_G-V_H) / R_{gain} = (V_1-V_2) / R_{gain}\dots\dots\dots(2)$$

Equating equations 1 and 2,

$$(V_{o1}-V_{o2})/(2R_1+R_{gain}) = (V_1-V_2)/R_{gain}$$

$$(V_{o1}-V_{o2}) = (2R_1+R_{gain})(V_1-V_2)/R_{gain} \dots\dots\dots(3)$$

The output of the difference amplifier is given as,

$$V_{out} = (R_3/R_2) (V_{o1}-V_{o2})$$


$$\text{Therefore, } (V_{o1} - V_{o2}) = (R_2/R_3)V_{out}$$

Substituting  $(V_{o1} - V_{o2})$  value in equation 3, we get

$$(R_2/R_3)V_{out} = (2R_1+R_{gain})(V_1-V_2)/R_{gain}$$

$$\text{i.e. } V_{out} = (R_3/R_2)\{(2R_1+R_{gain})/R_{gain}\}(V_1-V_2)$$

$$A_{cl} = R_3/R_2 (1+2R_1/R_{gain})$$

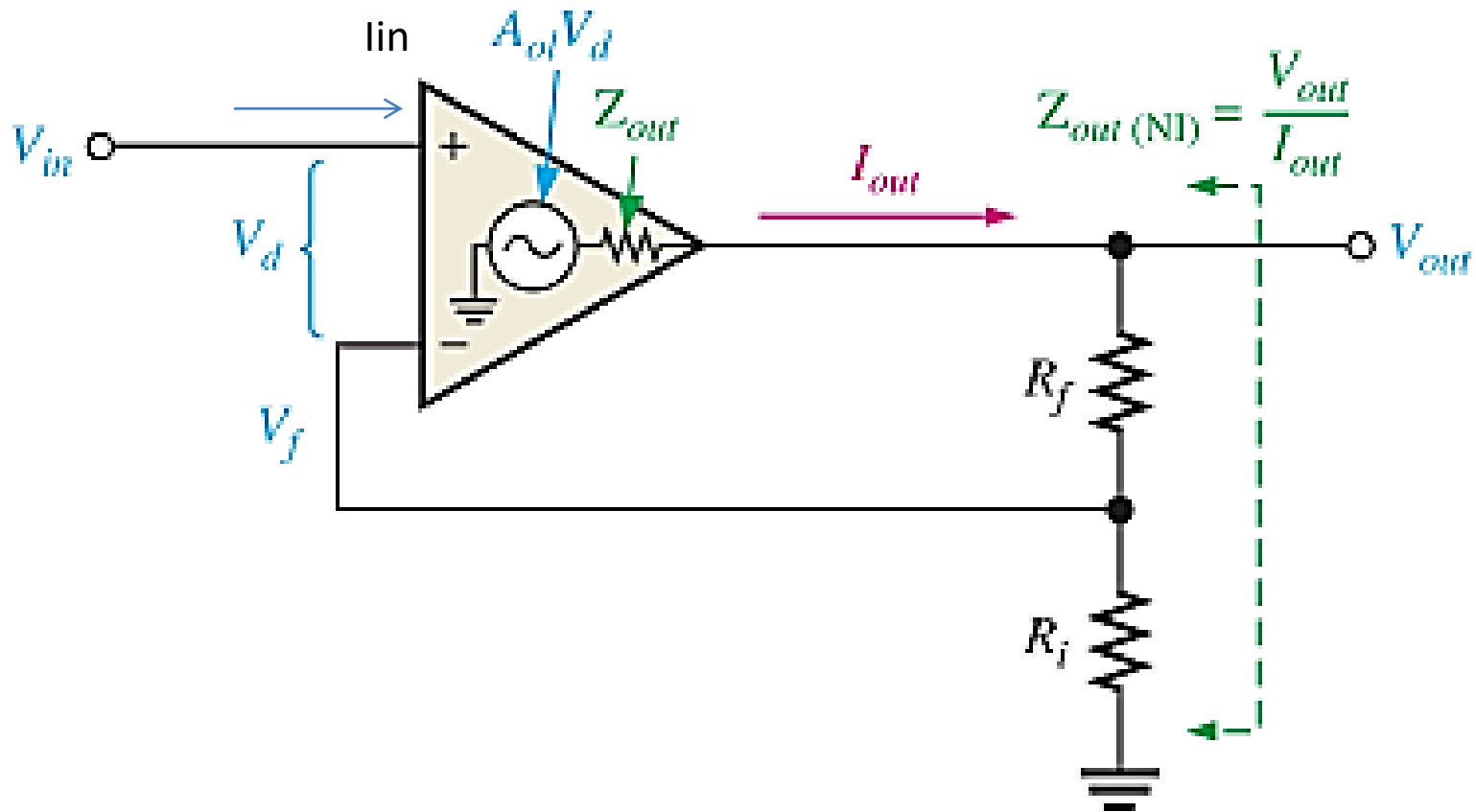

$V_d = I_{in} Z_{in}$   $Z_{in}$  - input impedance of op-amp in open loop condition

$v_{in} - v_f = v_d$


$v_f = B v_o$ ;  $B = \frac{R_i}{R_i + R_f}$ ;  $v_{out} = A_{ol} v_d$

$V_{in} = I_{in} Z_{in} (1 + B A_{ol})$

$Z_{in(NI)} = V_{in} / I_{in} = Z_{in} (1 + B A_{ol})$


$$Z_{out(NI)} = \frac{Z_{out}}{1 + A_{ol} B}$$

## Logarithmic amplifier

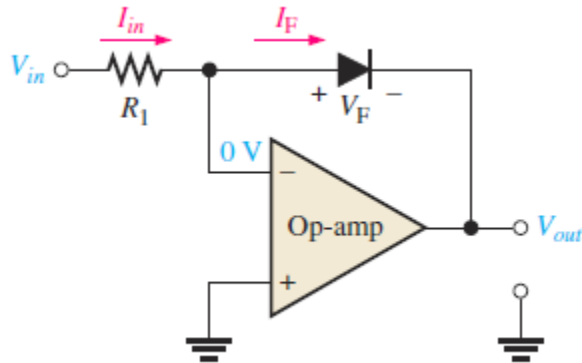

$$V_{out} = -V_F$$

$$I_F = I_{in} = \frac{V_{in}}{R_1}$$

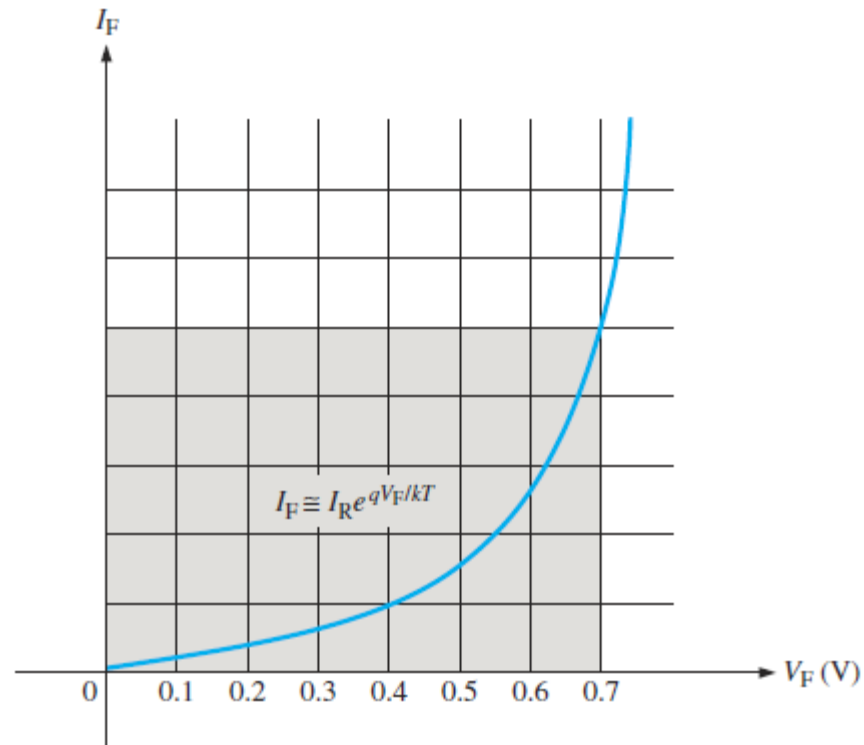

As you can see on the graph, the diode curve is nonlinear. Not only the curve is nonlinear, it is logarithmic and is specifically defined by the following equation:

$$I_F \cong I_R e^{qV_F/kT}$$

where  $I_R$  is the reverse leakage current,  $q$  is the charge on an electron,  $k$  is Boltzmann's constant, and  $T$  is the absolute temperature in Kelvin. From the previous equation, the diode forward voltage,  $V_F$ , can be determined as follows. Take the natural logarithm ( $\ln$  is the logarithm to the base  $e$ ) of both sides.

$$\ln I_F = \ln I_R e^{qV_F/kT}$$

The  $\ln$  of a product of two terms equals the sum of the  $\ln$  of each term.

$$\ln I_F = \ln I_R + \ln e^{qV_F/kT} = \ln I_R + \frac{qV_F}{kT}$$

$$\ln I_F - \ln I_R = \frac{qV_F}{kT}$$

The difference of two  $\ln$  terms equals the  $\ln$  of the quotient of the terms.

$$\ln\left(\frac{I_F}{I_R}\right) = \frac{qV_F}{kT}$$

$$V_{out} = -\left(\frac{kT}{q}\right) \ln\left(\frac{V_{in}}{I_R R_1}\right)$$

The **antilogarithm** of a number is the result obtained when the base is raised to a power equal to the logarithm of that number. To get the antilogarithm, you must take the exponential of the logarithm (antilogarithm of  $x = e^{\ln x}$ ).

An antilog amplifier is formed by connecting a transistor (or diode) as the input element as shown in Figure 14–33. The exponential formula still applies to the base-emitter *pn* junction. The output voltage is determined by the current (equal to the collector current) through the feedback resistor.

$$V_{out} = -R_f I_C$$

The characteristic equation of the *pn* junction is

$$I_C = I_{EBO} e^{qV_{BE}/kT}$$

Substituting into the equation for  $V_{out}$ ,

$$V_{out} = -R_f I_{EBO} e^{qV_{BE}/kT}$$

As you can see in Figure 14–33,  $V_{in} = V_{BE}$ .

$$V_{out} = -R_f I_{EBO} e^{qV_{in}/kT}$$

The exponential term can be expressed as an antilogarithm as follows:


$$V_{out} = -R_f I_{EBO} \text{antilog} \left( \frac{V_{in} q}{kT} \right)$$




Since  $kT/q$  is approximately 25 mV,

$$V_{out} = -R_f I_{EBO} \text{antilog} \left( \frac{V_{in}}{25 \text{ mV}} \right)$$

► **FIGURE 14–33**


A basic antilog amplifier.

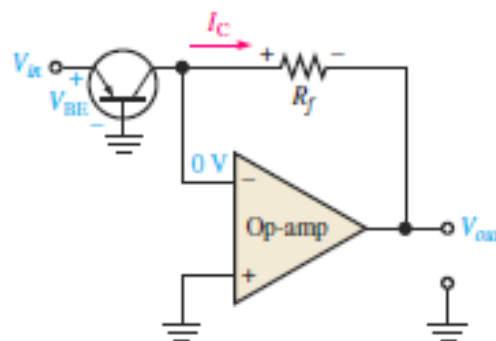

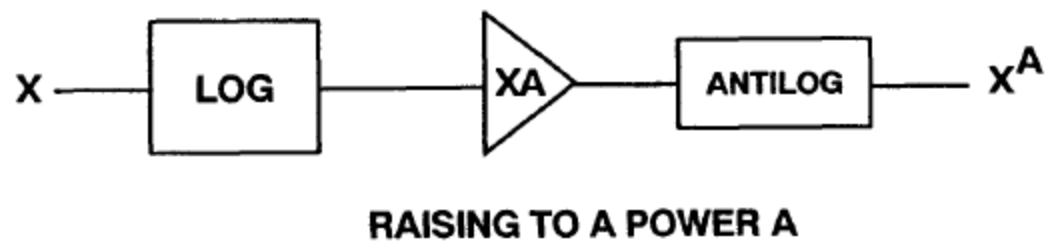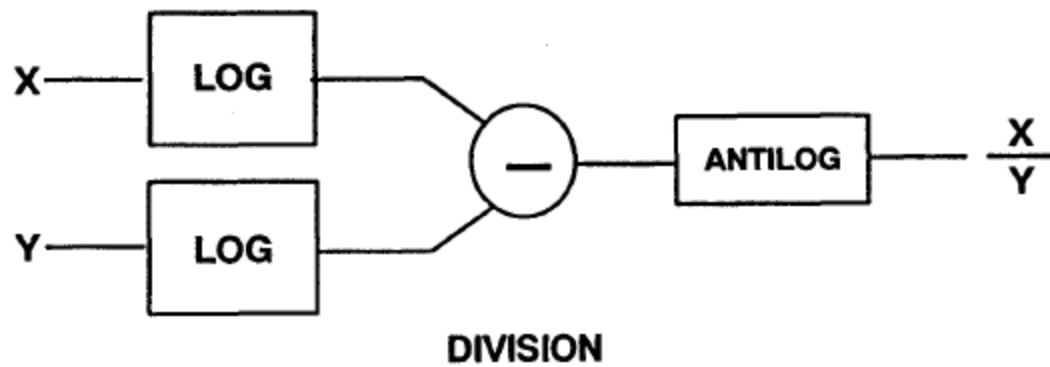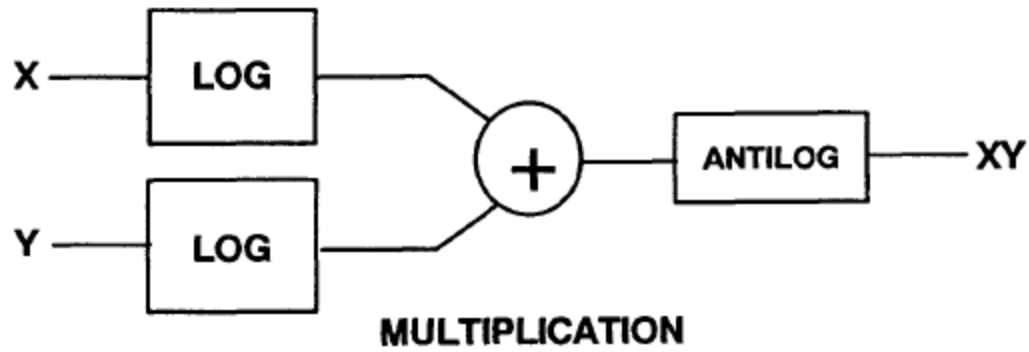


Trans-resistance amplifier  $\rightarrow$  current dependent voltage source  
 $R = V_{out}/I_{in}$


# Half-wave rectifier

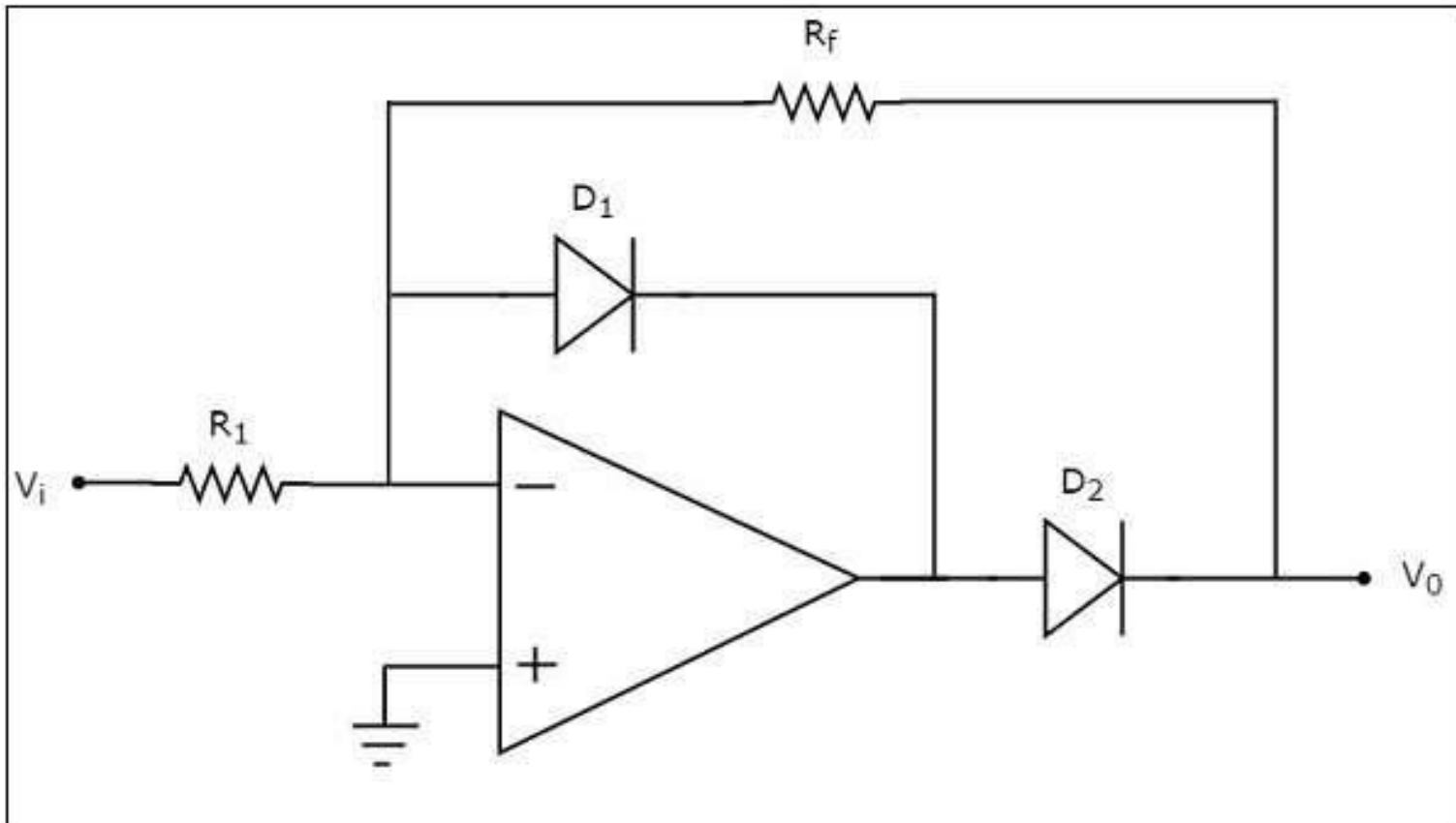

Sinusoidal Input Signal

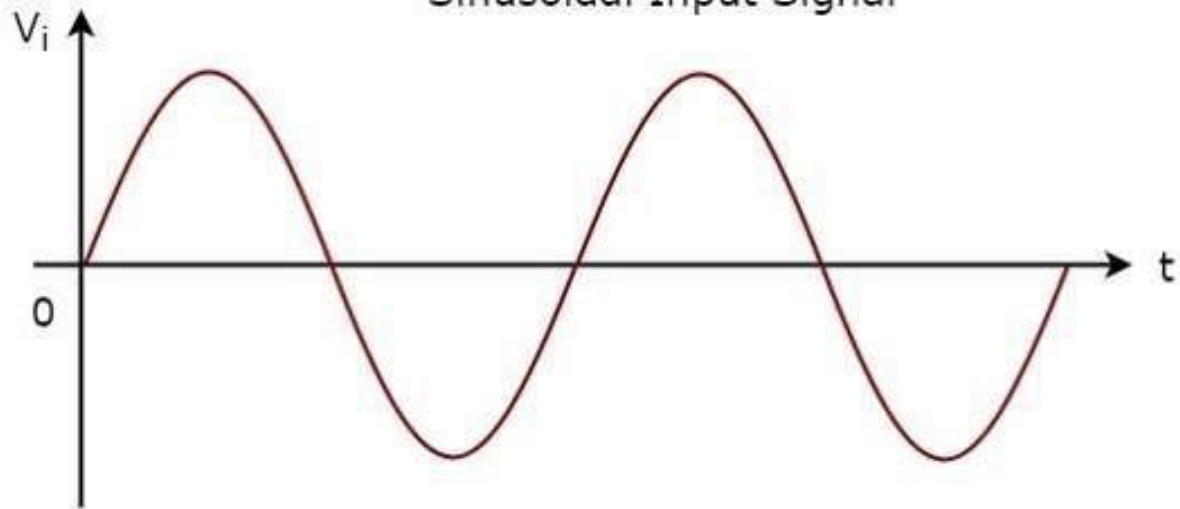


Output Signal

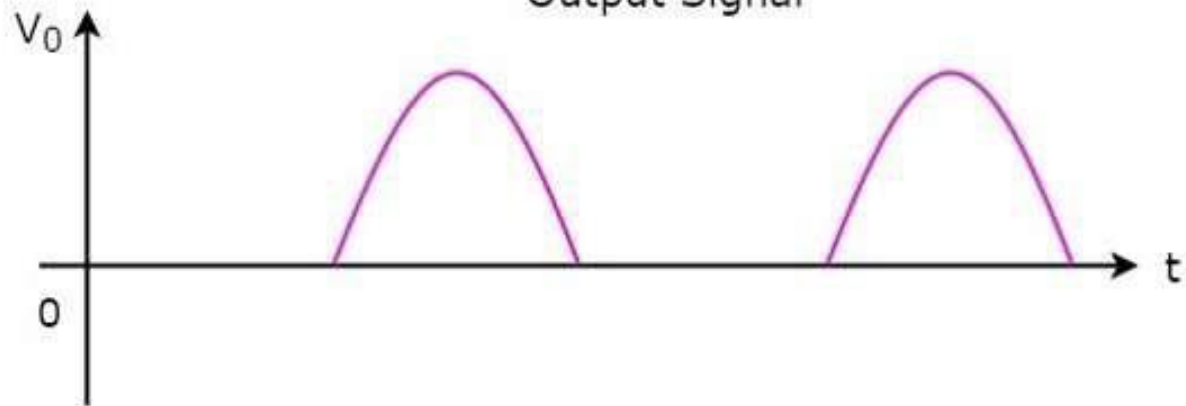


$$V_{o+} = v_i R_2 / R_1 \quad R_5 / R_4$$
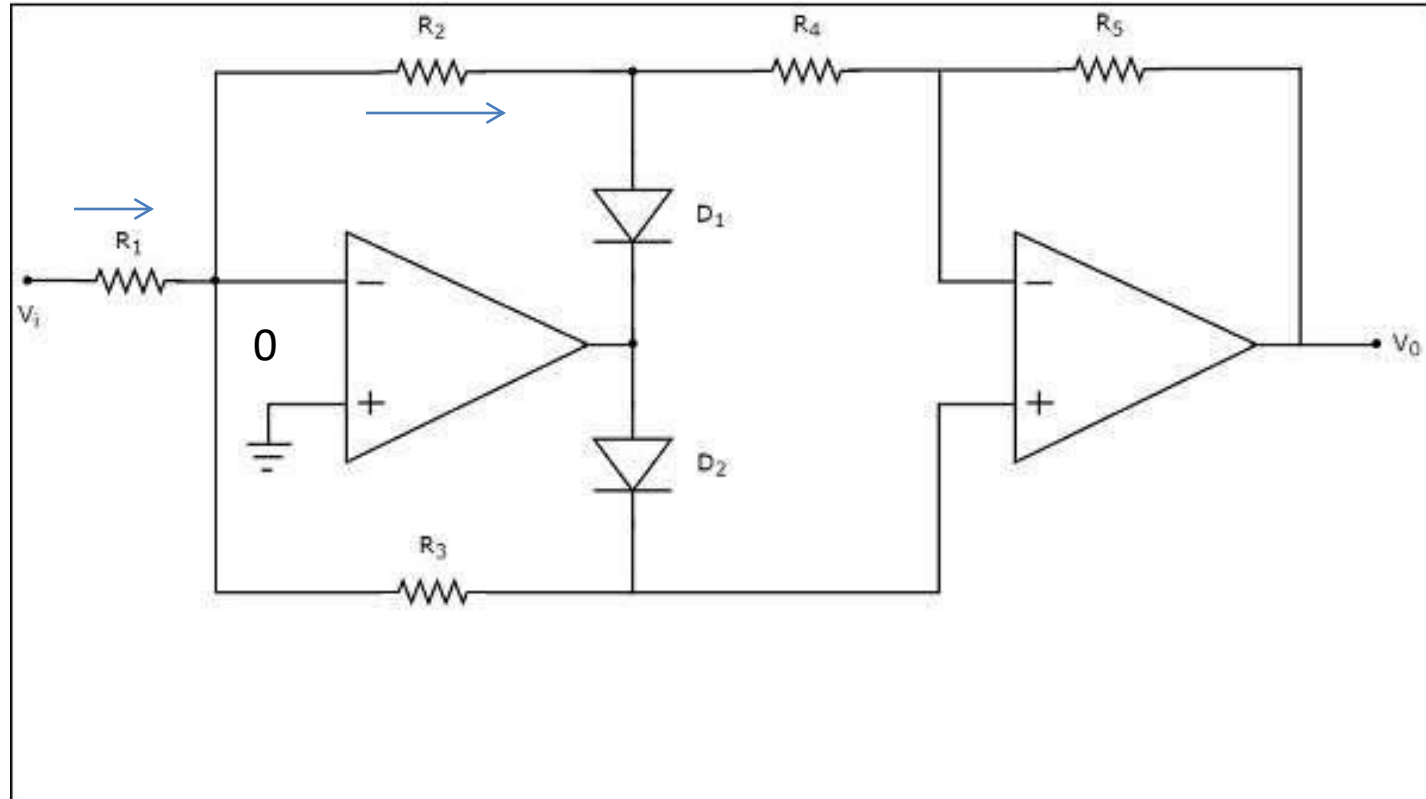
$$V_{o-} = -v_i R_3 / R_1 (1 + R_5 / R_4)$$





$$V_{o1} = - \left( \frac{R_2}{R_1} \right) V_i$$

Sinusoidal Input Signal

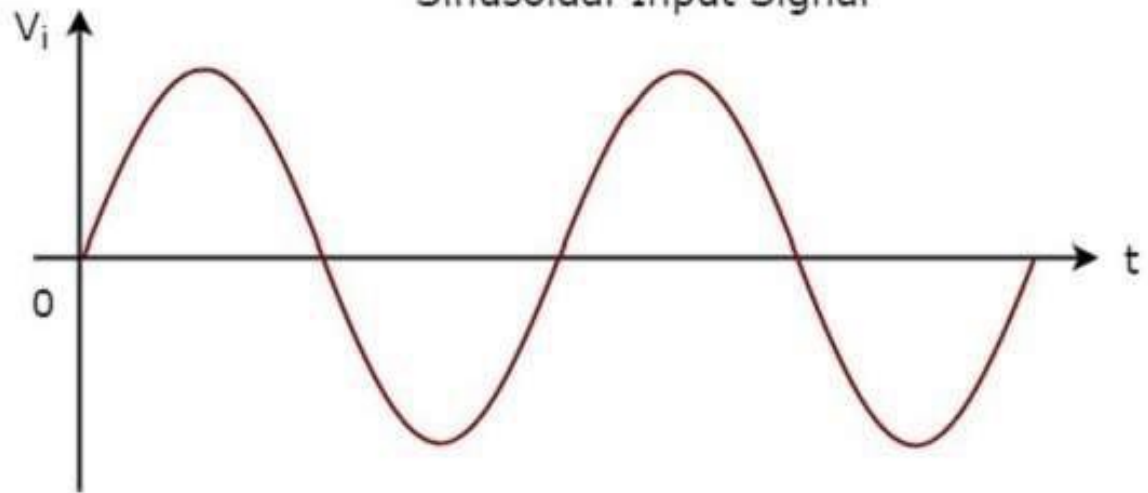

Output Signal

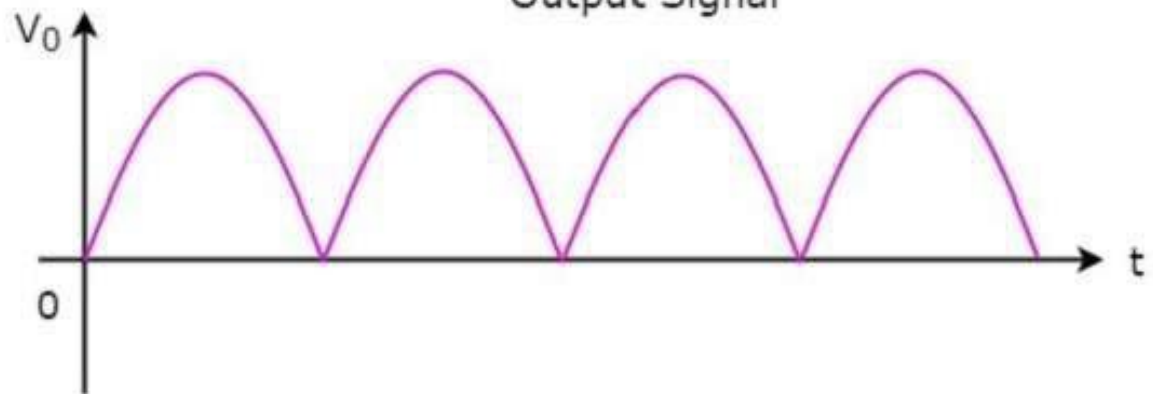

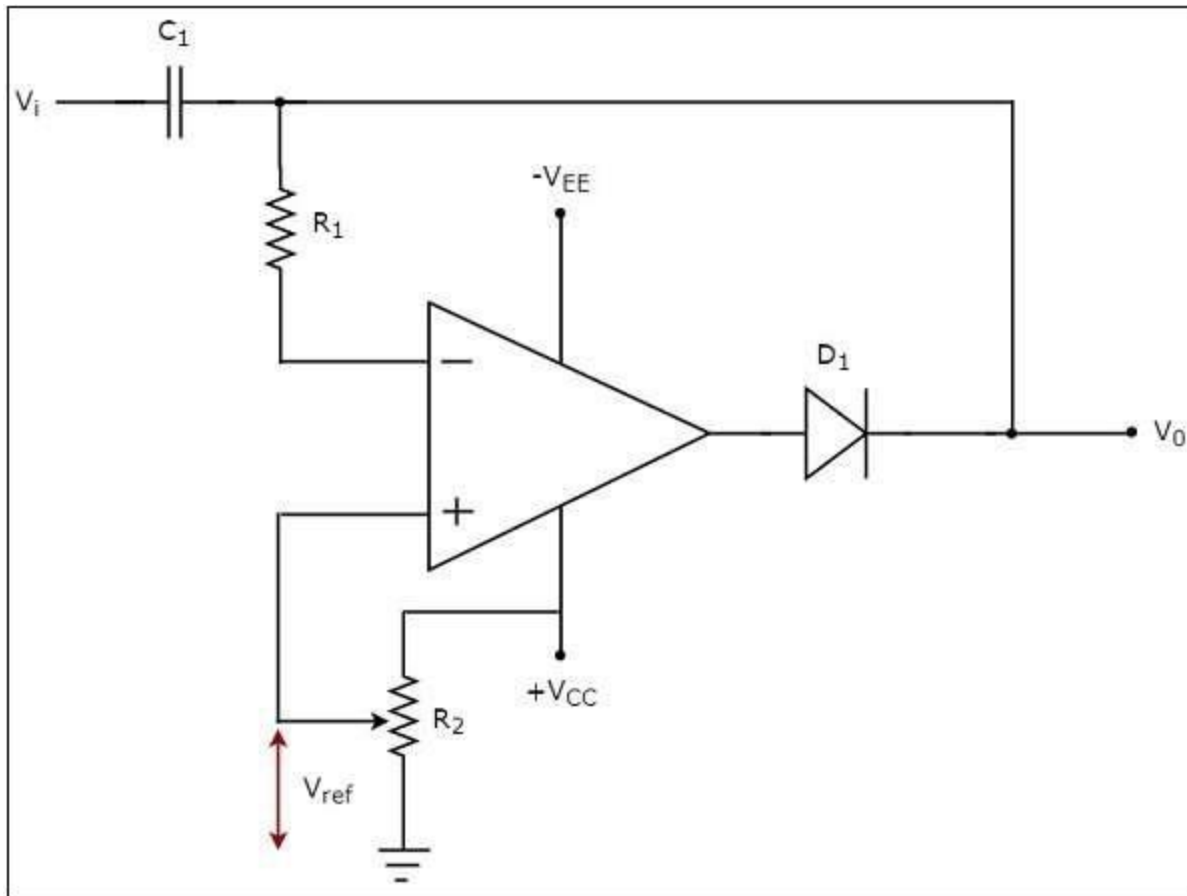

2:15 PM

001910701012

Sagnik Banerjee

2:15 PM

001910701015

sagar sarkar

2:15 PM

001910701041

Arijit Saha

2:15 PM

001910701019

Utso Majumder

2:15 PM

001910701070

You

2:15 PM

\G1 join at 3:15 pm

Tandeep Singh

2:15 PM

001910701002

Snehasish Roy

2:15 PM


Snehasish Roy 001910701013


Souvik Barman

2:15 PM



001910701070


## Clampers

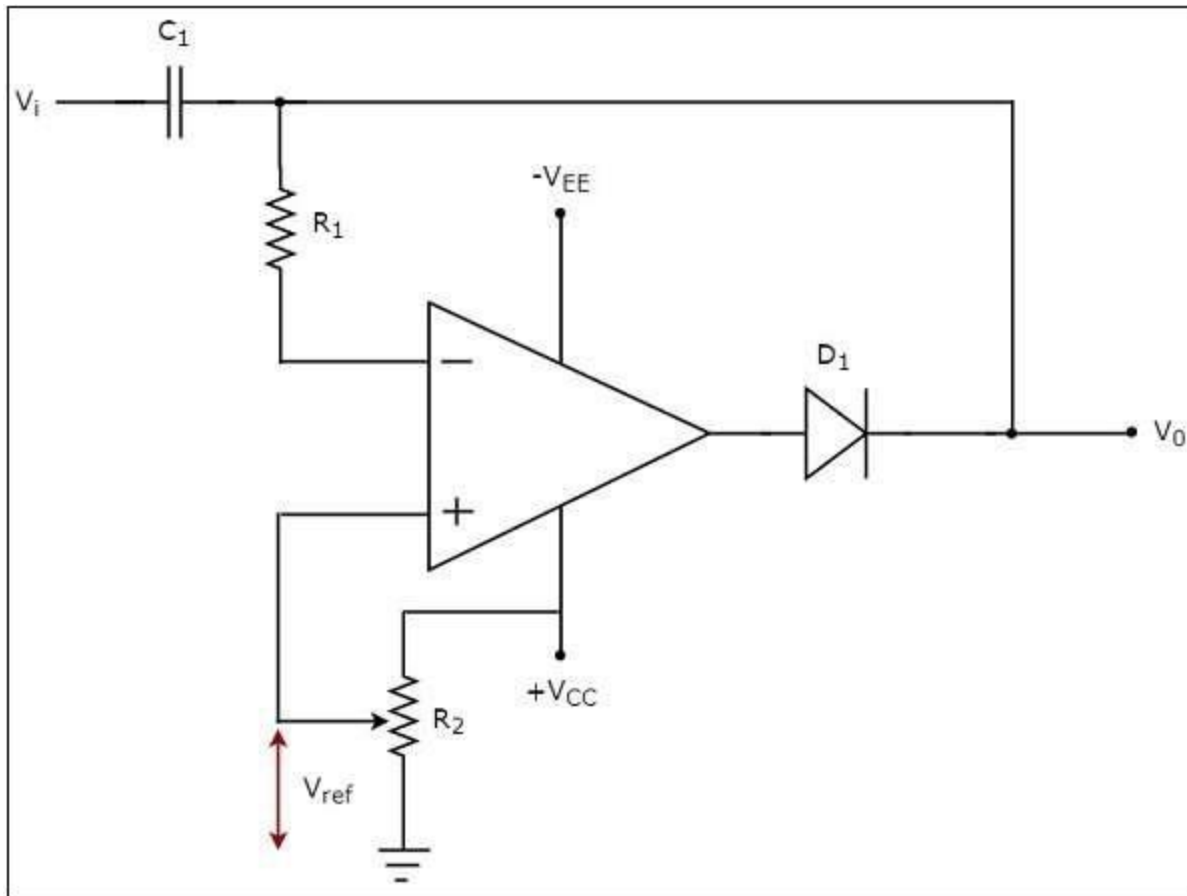


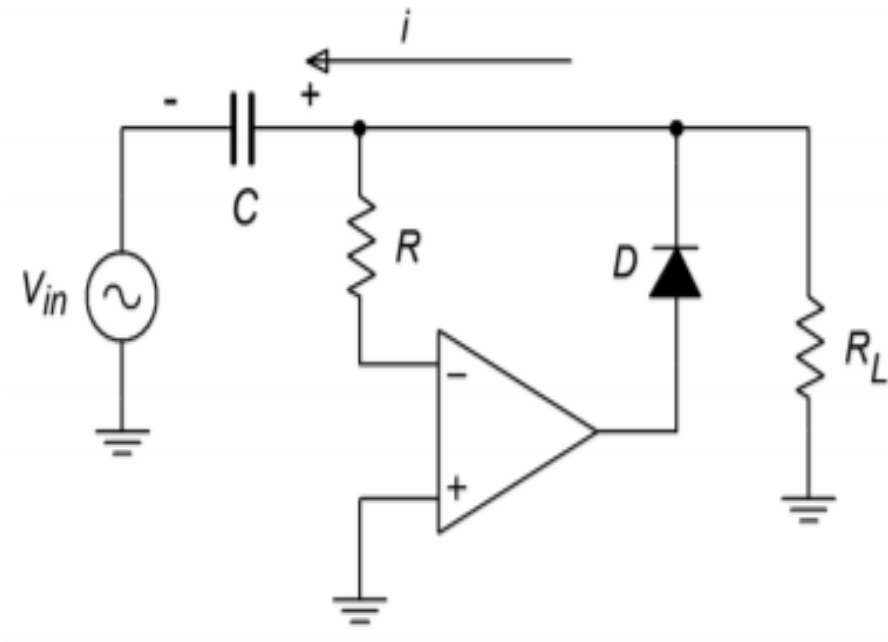



$$V_{out} = V_{in} + |V_{p^-}| + V_{ref}$$

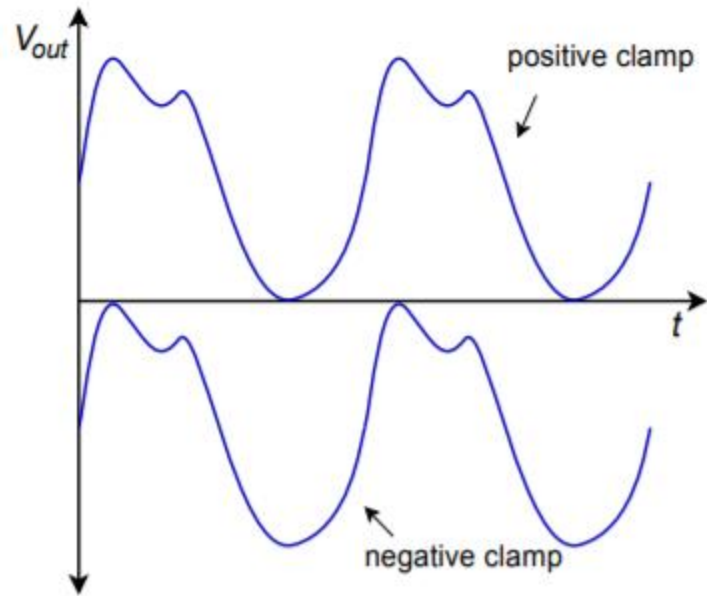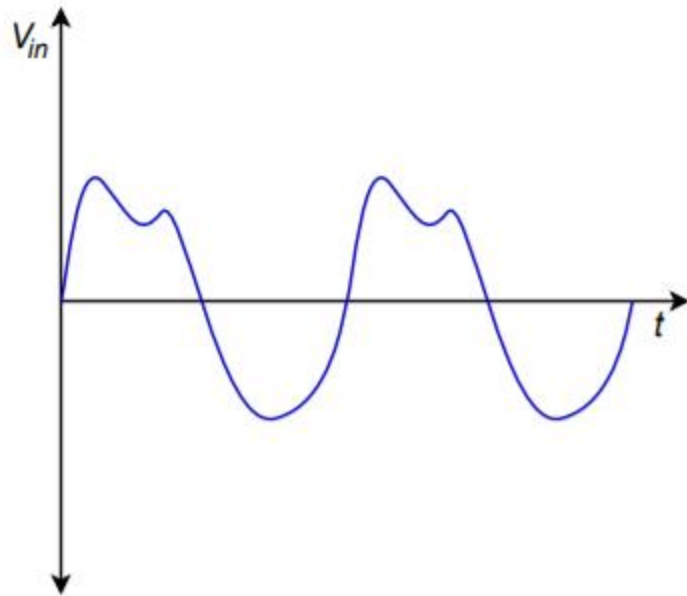


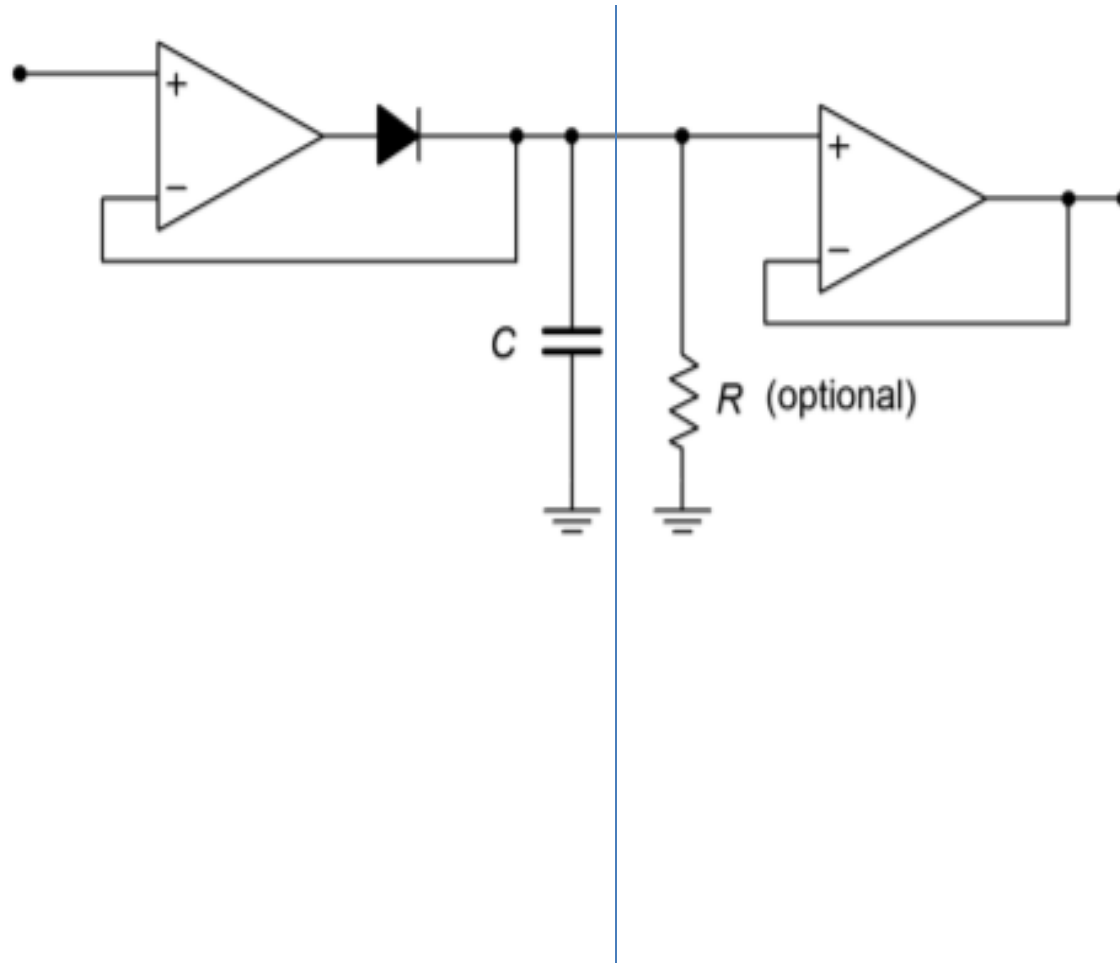


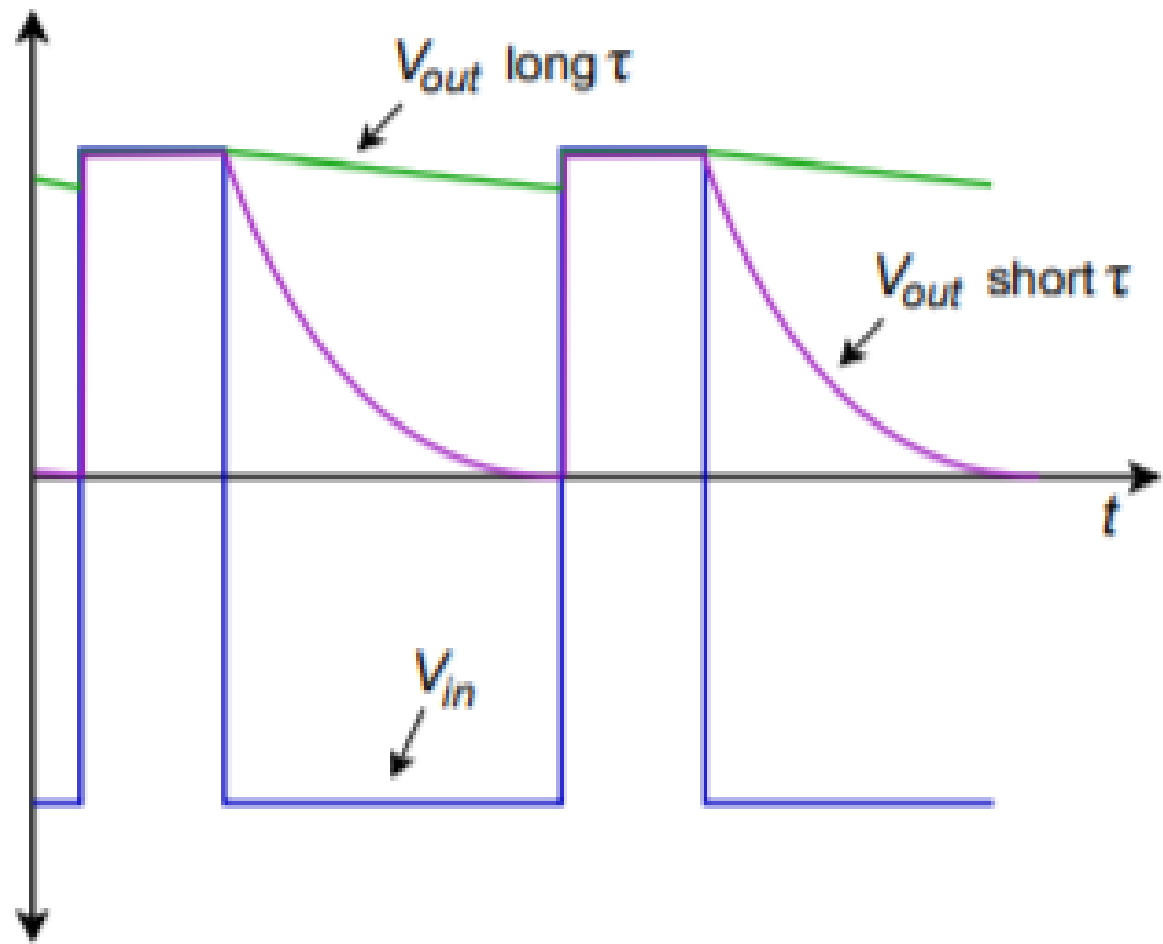


# Zero crossing detector

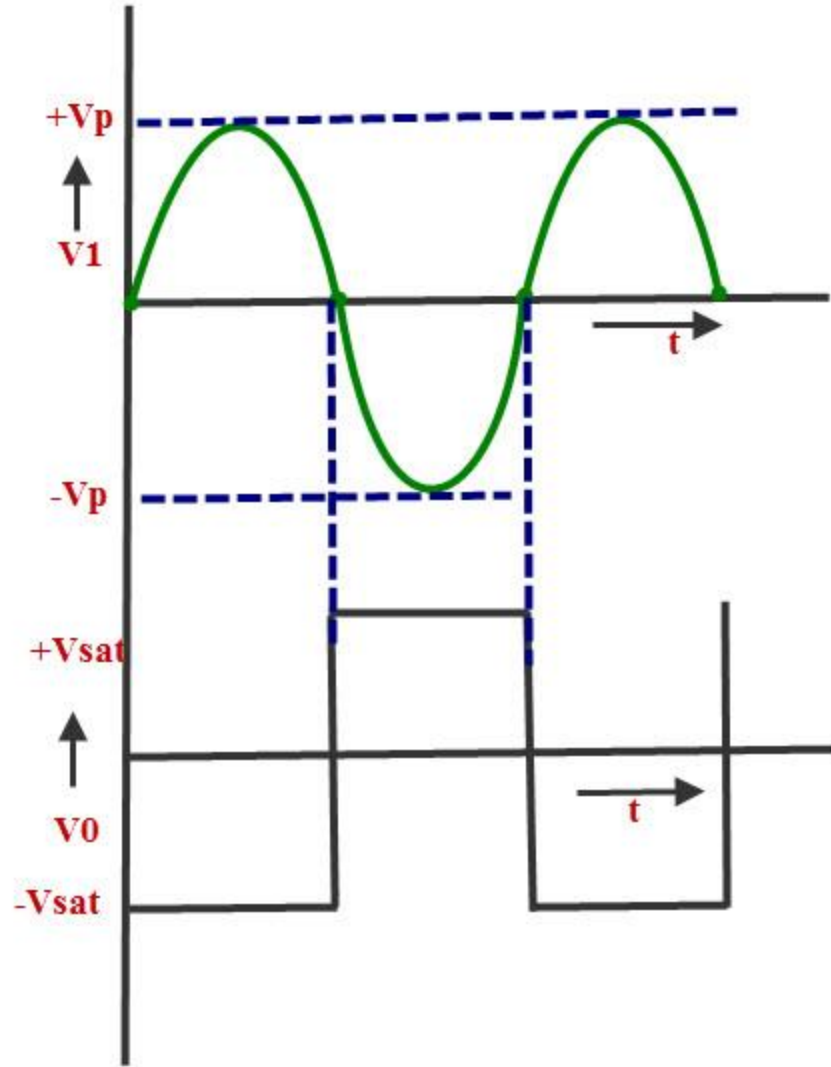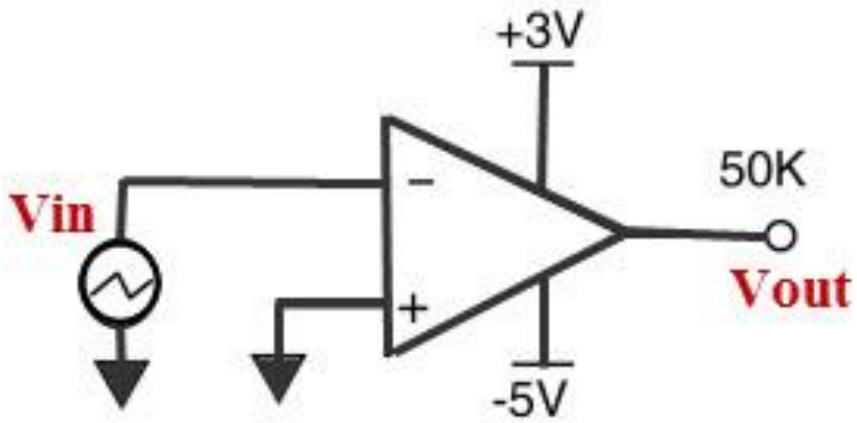



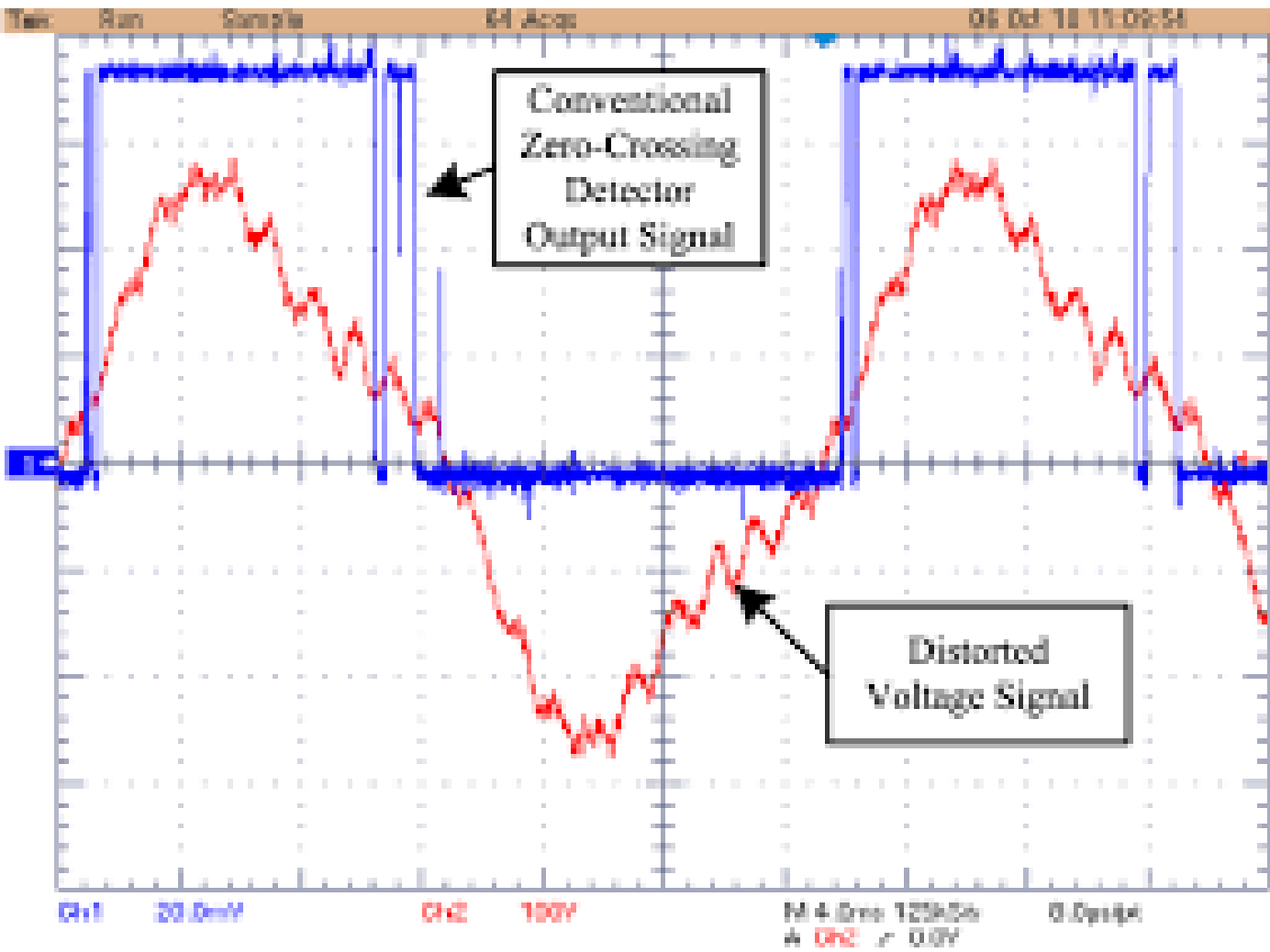


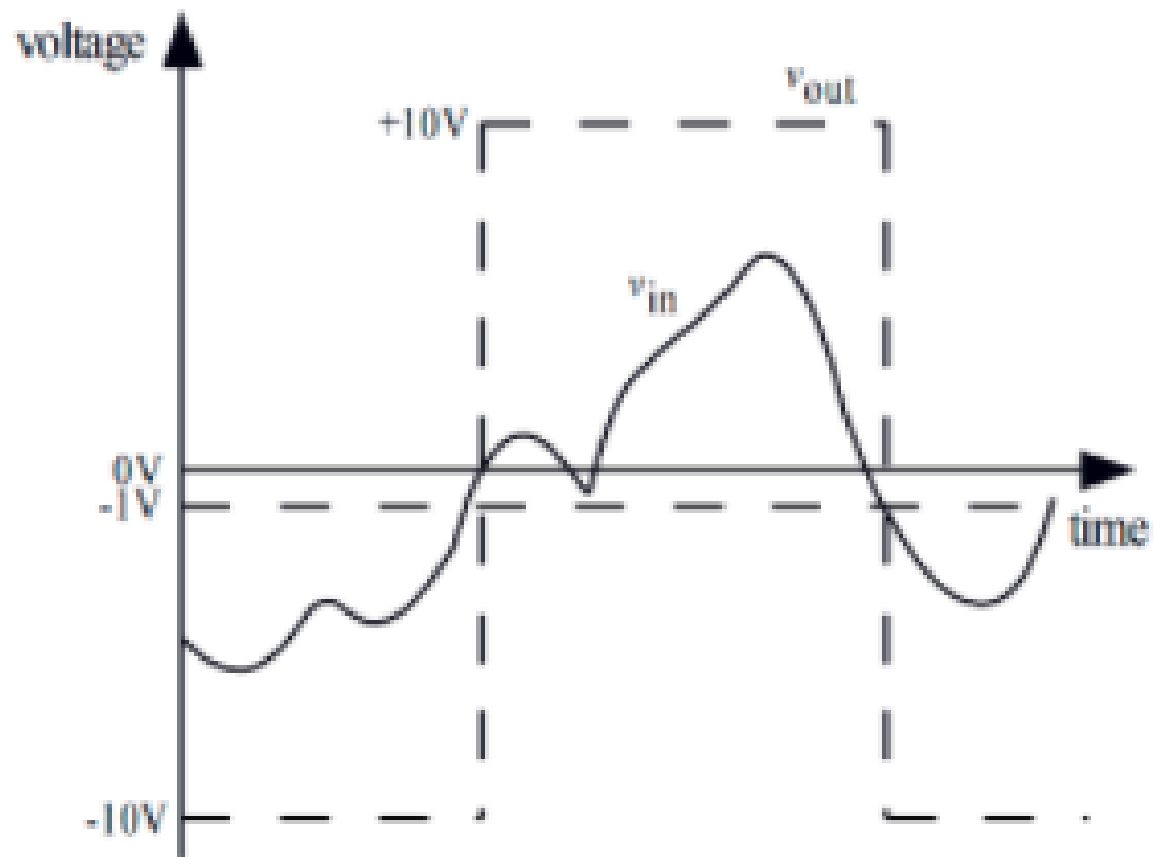

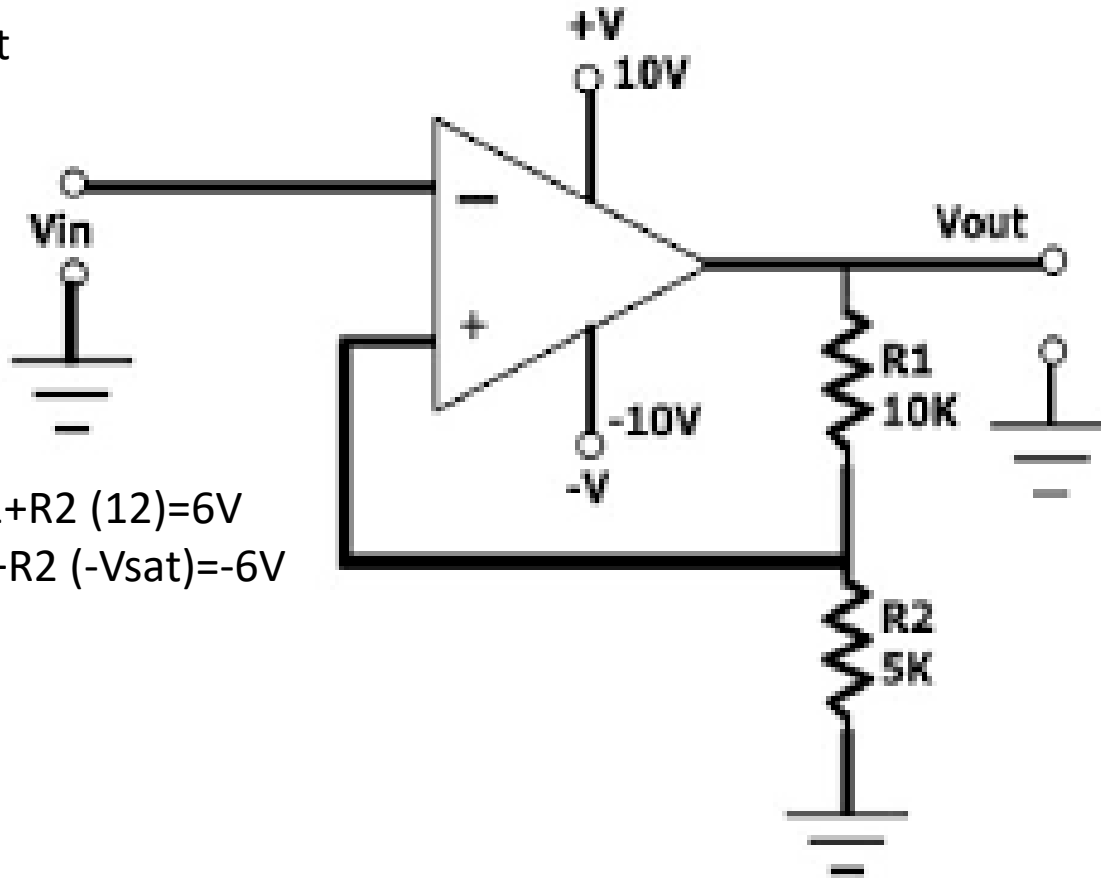$V > V^+ \quad v_{out} = -V_{sat}$   
 $V < V^+ \quad v_{out} = V_{sat}$



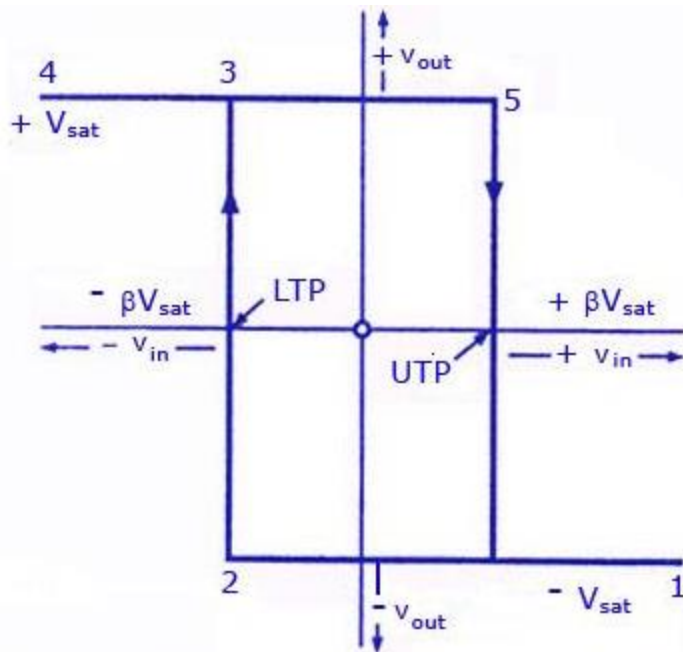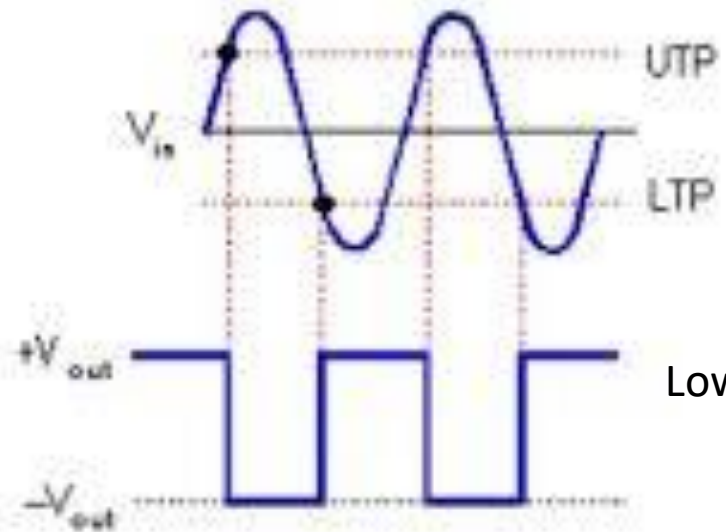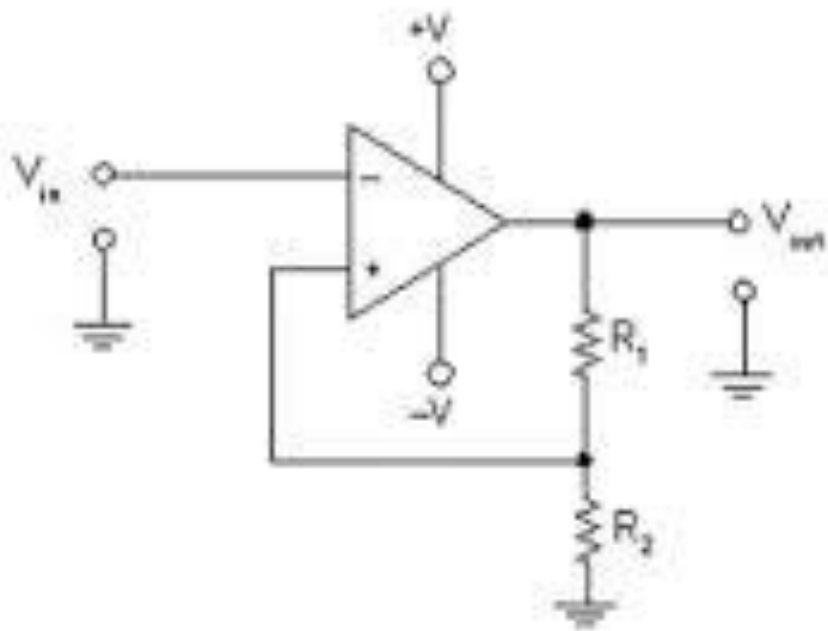$UTP = V_{ref}^+ = \frac{R_2}{R_1 + R_2} (12) = 6V$   
 $LTP = V_{ref}^- = \frac{R_2}{R_1 + R_2} (-V_{sat}) = -6V$



Input Output Characteristics